

HIGH-EFFICIENCY RF POWER AMPLIFIERS AND TRANSMITTERS


Frederick H. Raab, Ph.D.

Green Mountain Radio Research Company
f.raab@ieee.org


- 1. Introduction**
- 2. Power Amplifiers**
- 3. Architectures**

AMPLIFIERS vs. ARCHITECTURES


CLASS-A PA

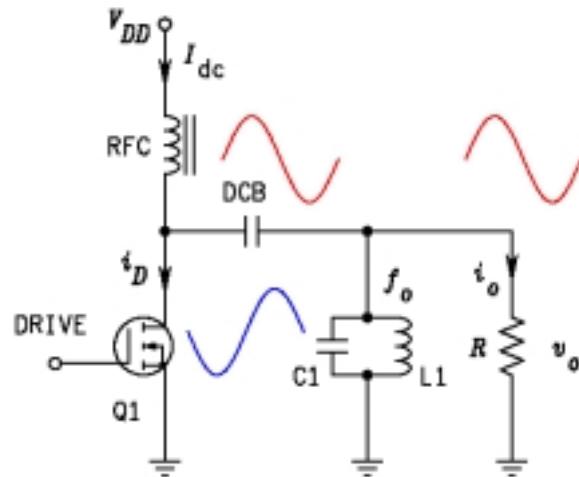


LINEAR ARCHITECTURE

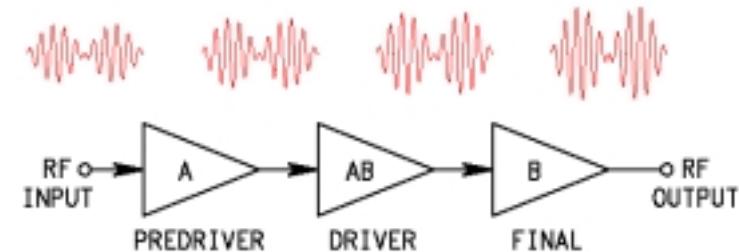

CLASS-F PA

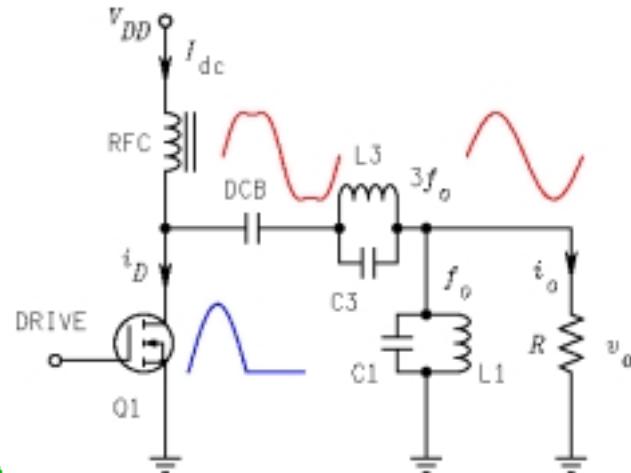


KAHN ARCHITECTURE

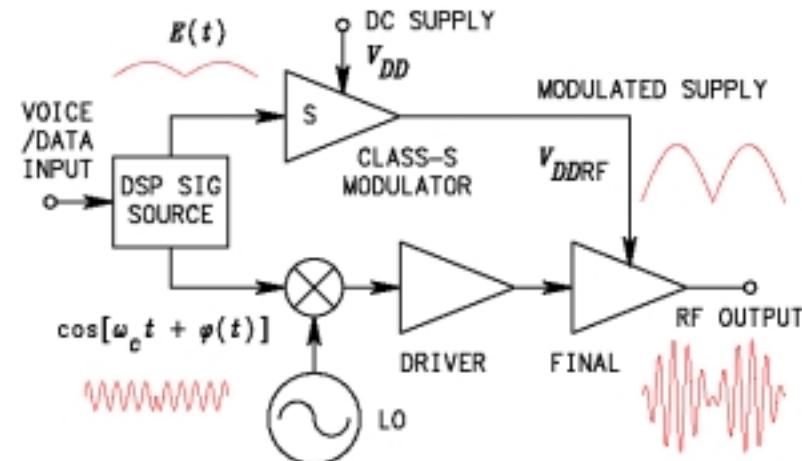


INSTANTANEOUS EFFICIENCY

LINEAR-AMPLIFIER CHAIN

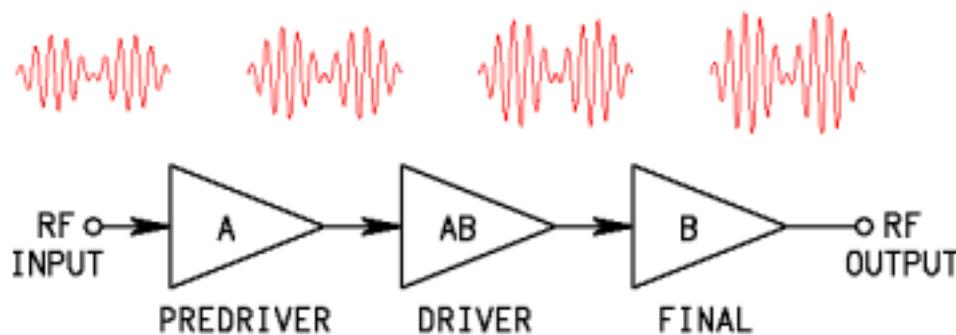

INSTANTANEOUS EFFICIENCY

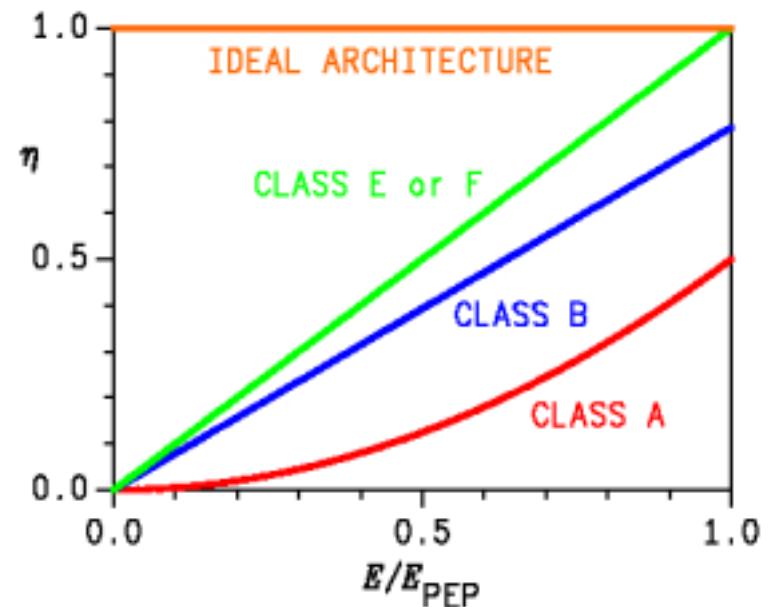


$$\eta = P_o / P_i$$

$$\eta_A = (P_o - P_{DR}) / P_i$$


$$\eta_O = P_o / (P_i + P_{DR})$$

AVERAGE EFFICIENCY


SRRC

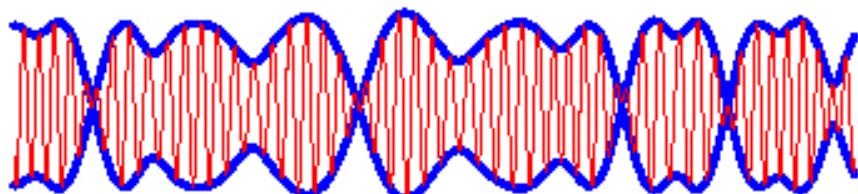

OFDM

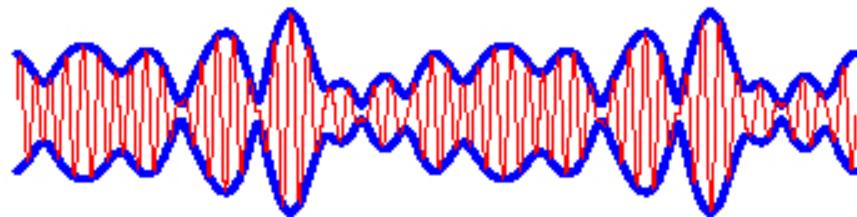

ENVELOPE PDF

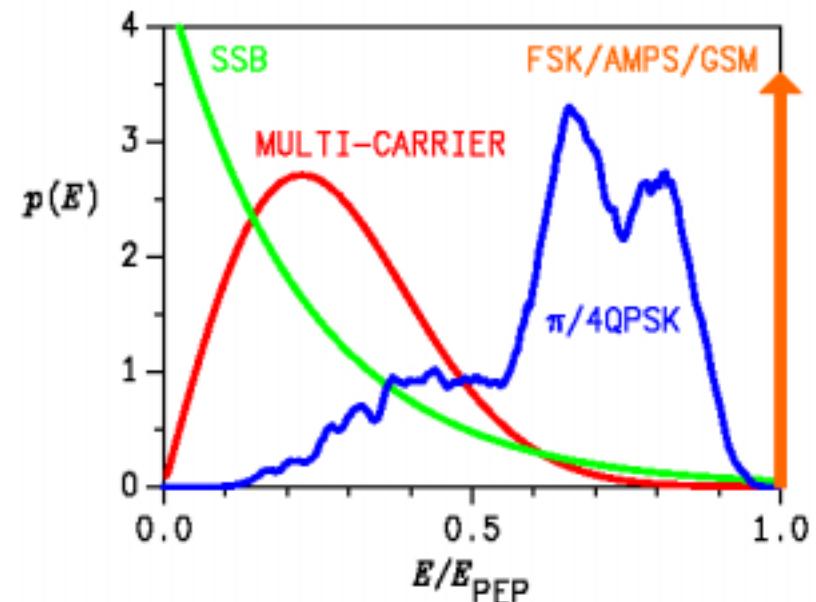


- Low amplitudes more likely
- Low average efficiency


$$\eta_{\text{AVG}} = \frac{P_{o\text{AVG}}}{P_{i\text{AVG}}}$$

DYNAMIC POWER RANGE

MOBILE-BASE GEOMETRY

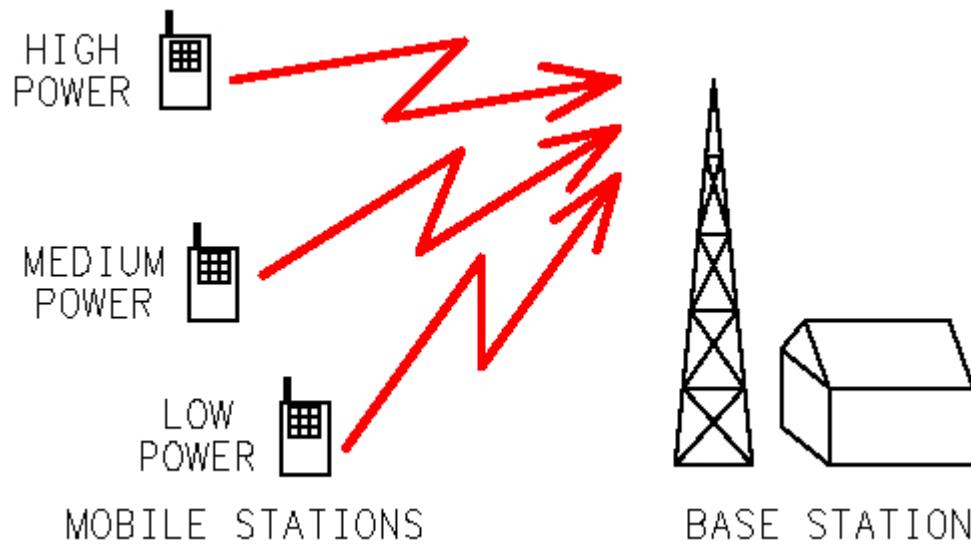

PDF OF PEP OUTPUT

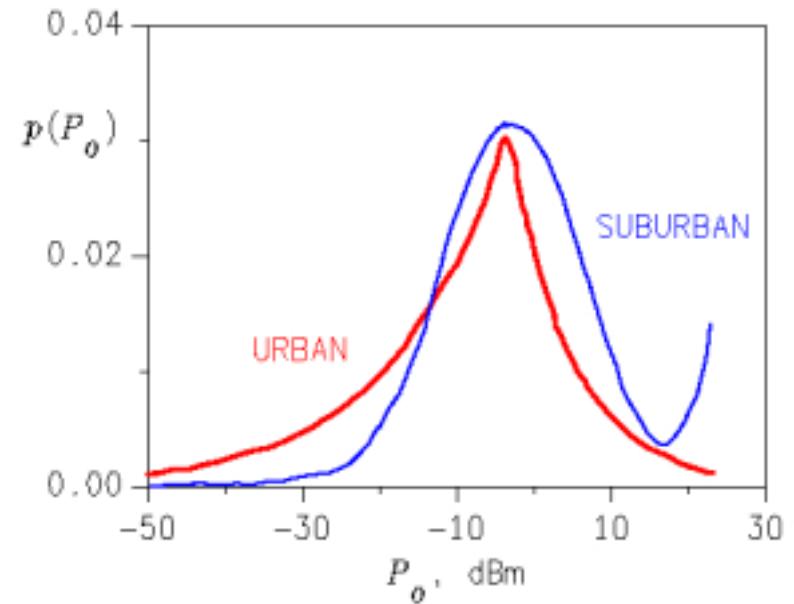

- Use minimum power
- Wide range of PEP output

RF-POWER AMPLIFIERS

CONVENTIONAL

HIGH EFFICIENCY

- CLASS A
- CLASS B
- CLASS C

- CLASS D
- CLASS E
- CLASS F

EFFICIENCY


$$\eta = P_o / P_i$$

UTILIZATION FACTOR


$$P_{\max} = \frac{P_{o\max}}{V_{D\max} i_{D\max}}$$

CLASS-A POWER AMPLIFIER

CIRCUIT

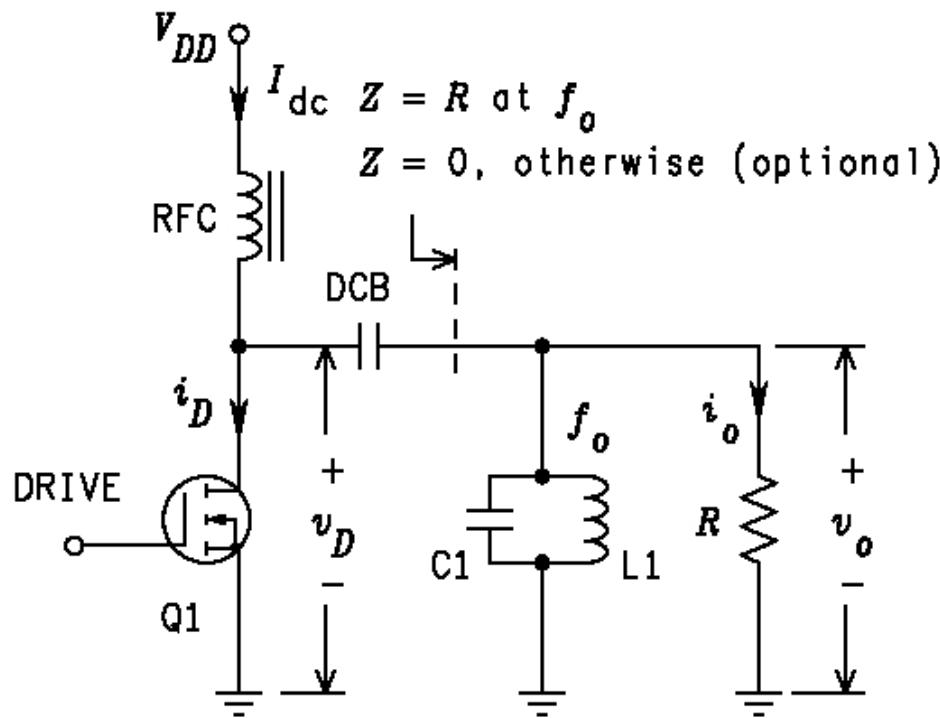


WAVEFORMS

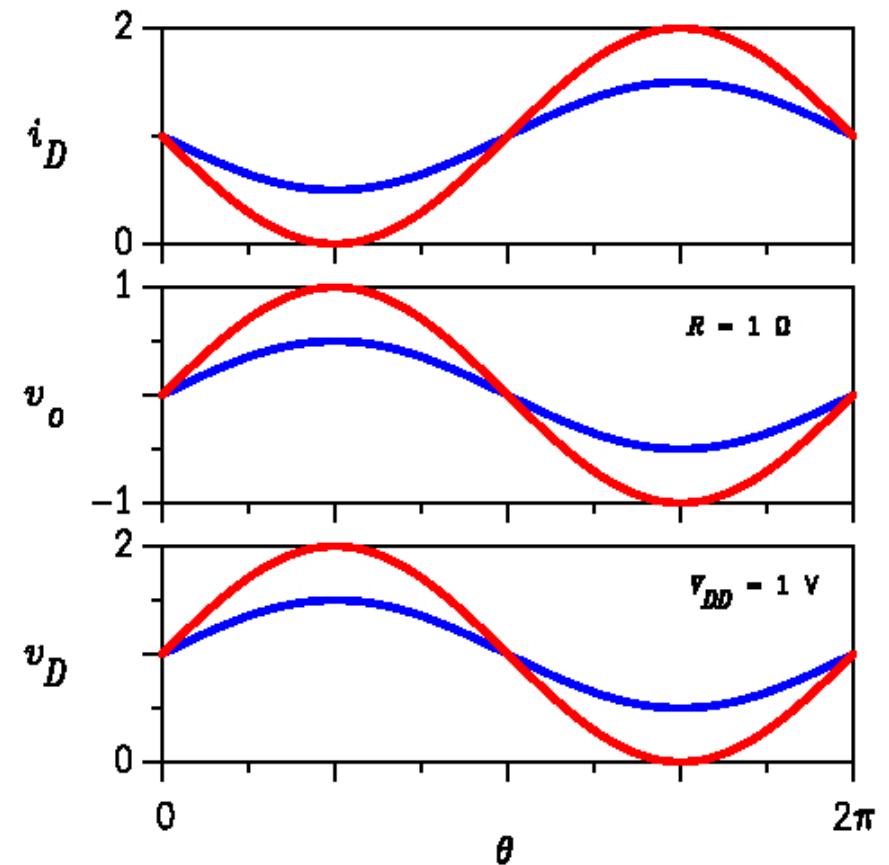


- $i_D > 0$ (360° conduction)
- No harmonics
- Output filter optional

CLASS A POWER AND EFFICIENCY

POWER

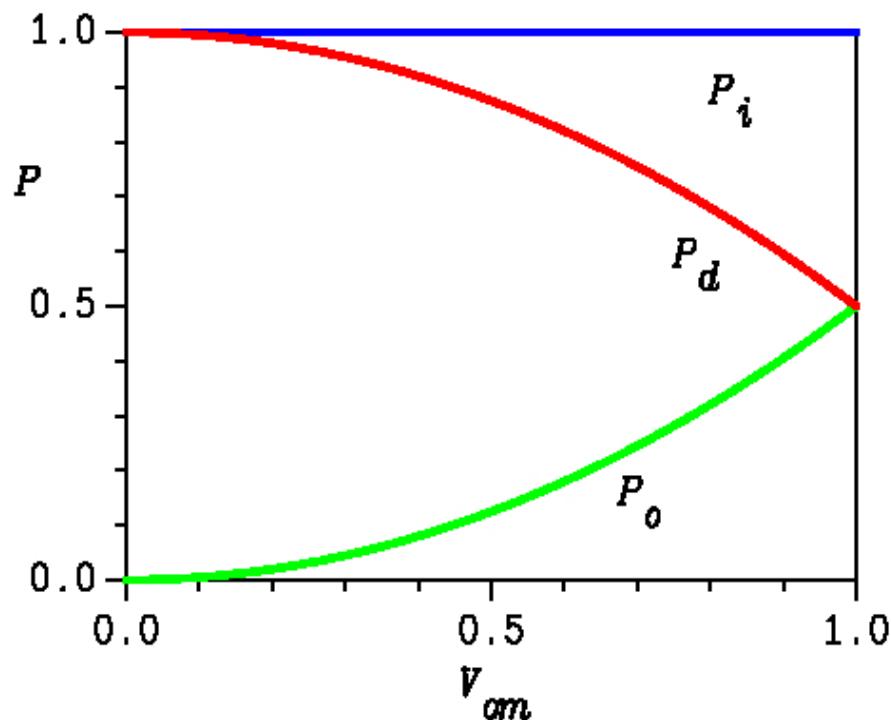

EFFICIENCY

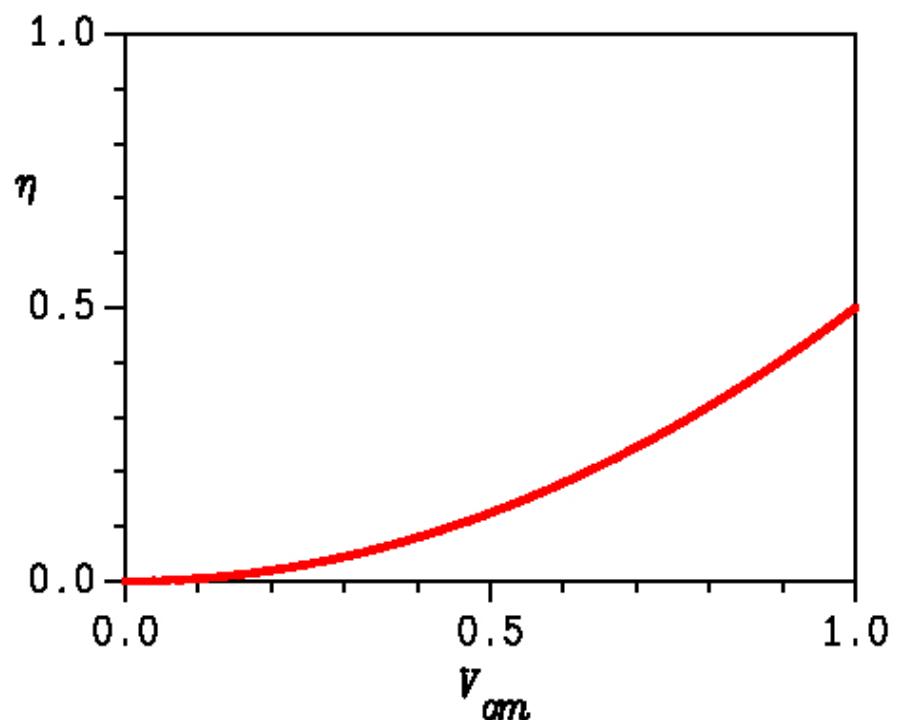


- Ideal transistors
- $V_{DD} = 1, R = 1$

- Efficiency \sim output power
- $\eta_{\text{PEP}} = 1/2 = 0.5$


$$P_{\max} = 0.125$$

CLASS-B POWER AMPLIFIER

CIRCUIT

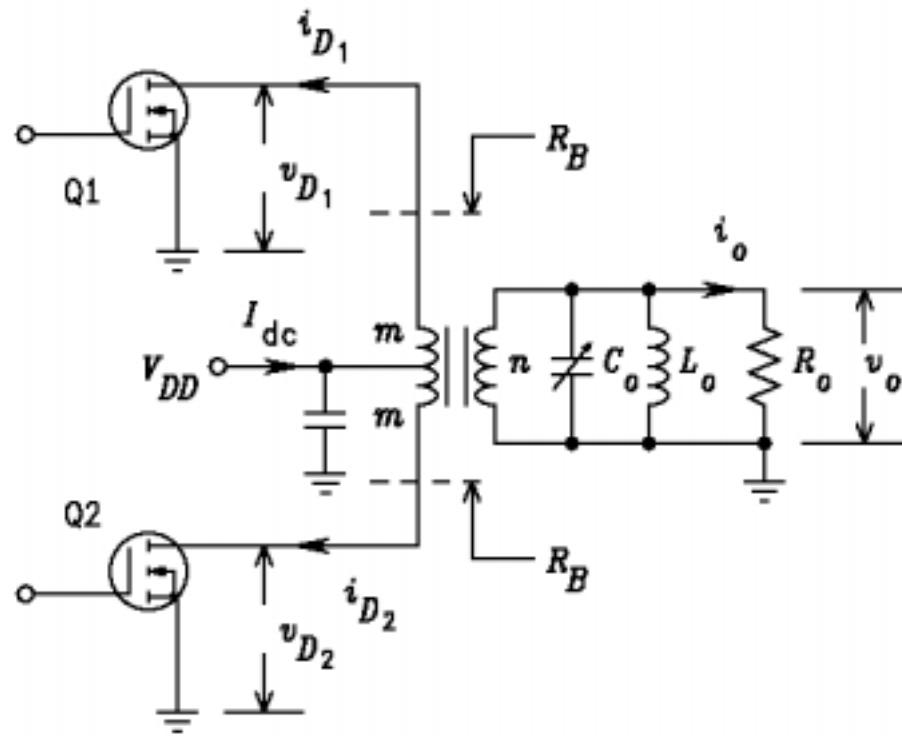


WAVEFORMS

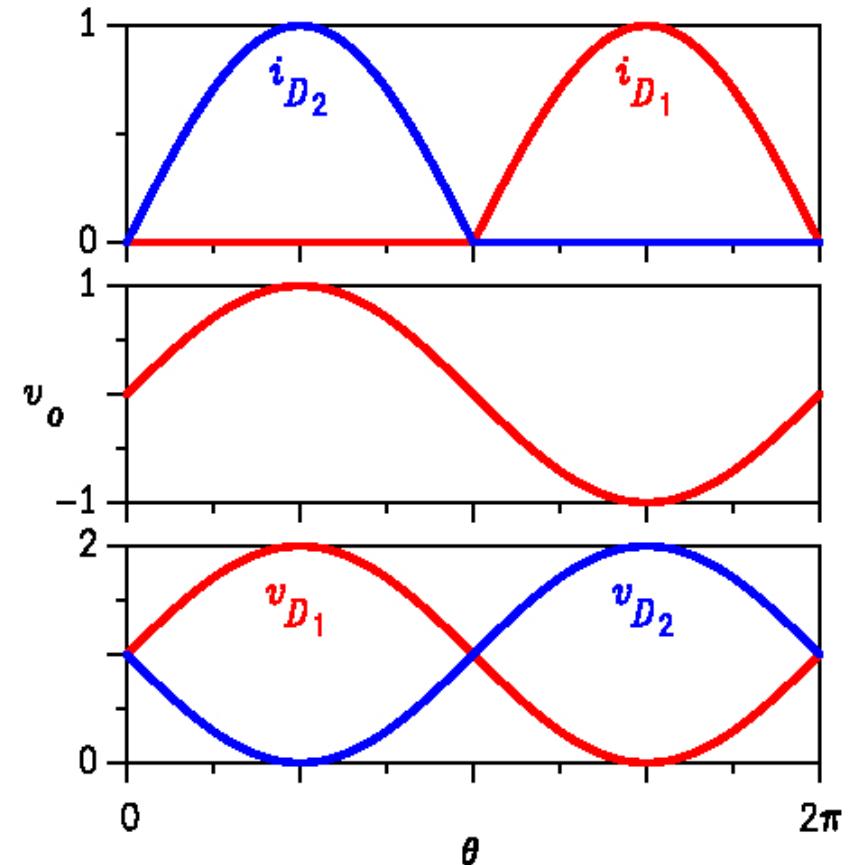


- $R_B = (m/n)^2 R_o$
- Q1 and Q2 conduct alternately
- $\approx 180^\circ$ conduction angle

CLASS B POWER AND EFFICIENCY

POWER

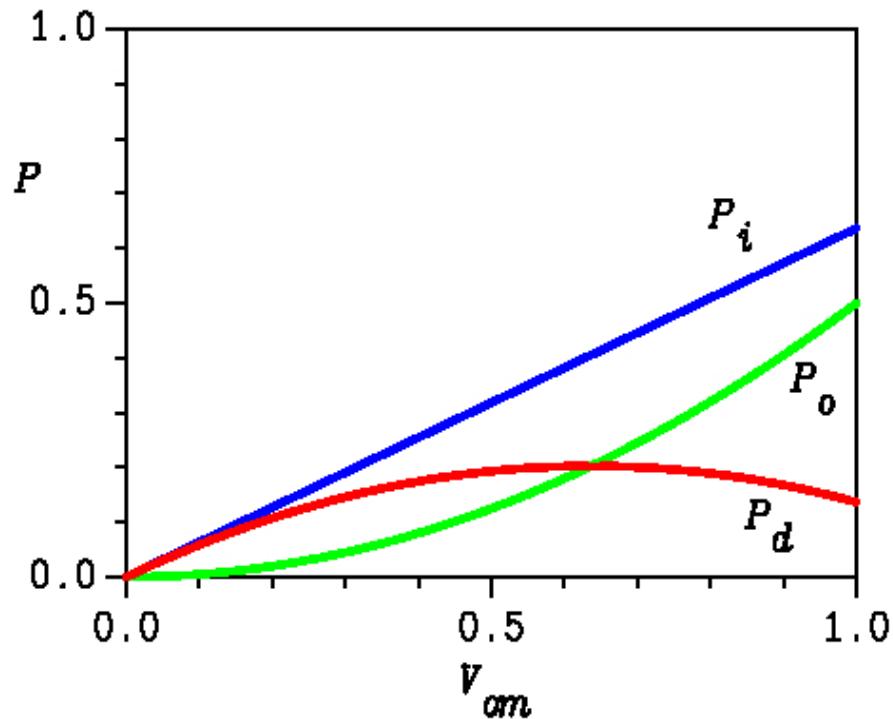

EFFICIENCY

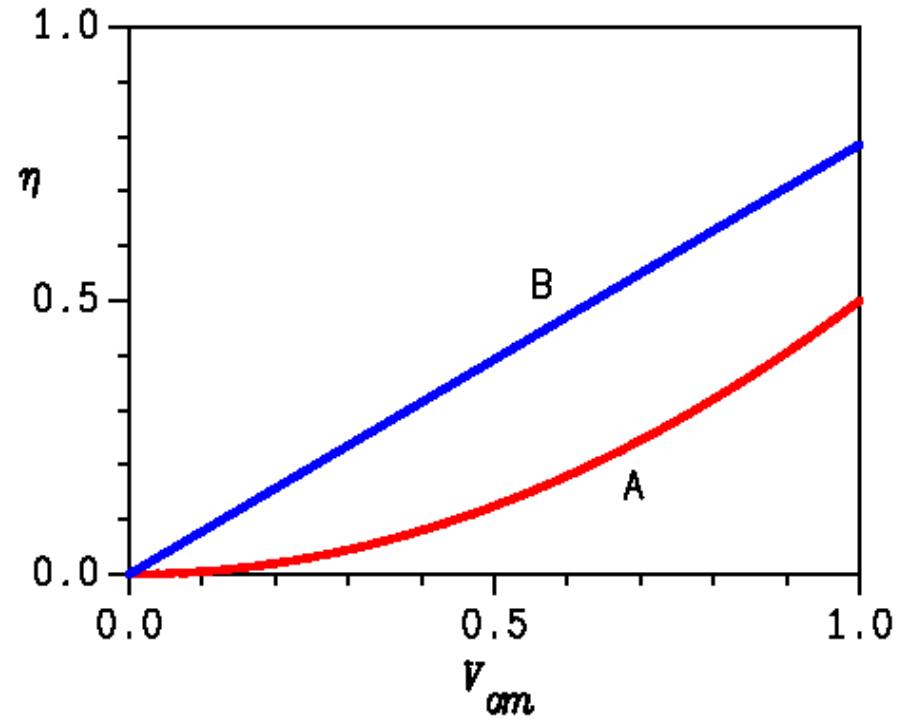


- Ideal transistors
- $V_{DD} = 1, R = 1$

- Efficiency \sim output voltage
- $\eta_{\text{PEP}} = \pi/4 = 0.785$


$$P_{\max} = 0.25$$

CLASS-C POWER AMPLIFIER

CIRCUIT

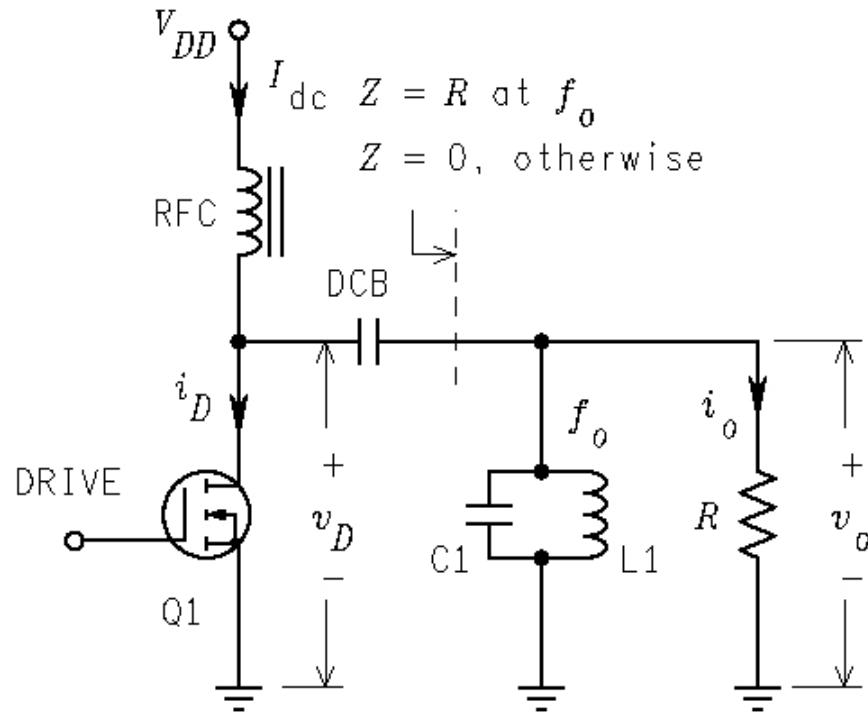


WAVEFORMS

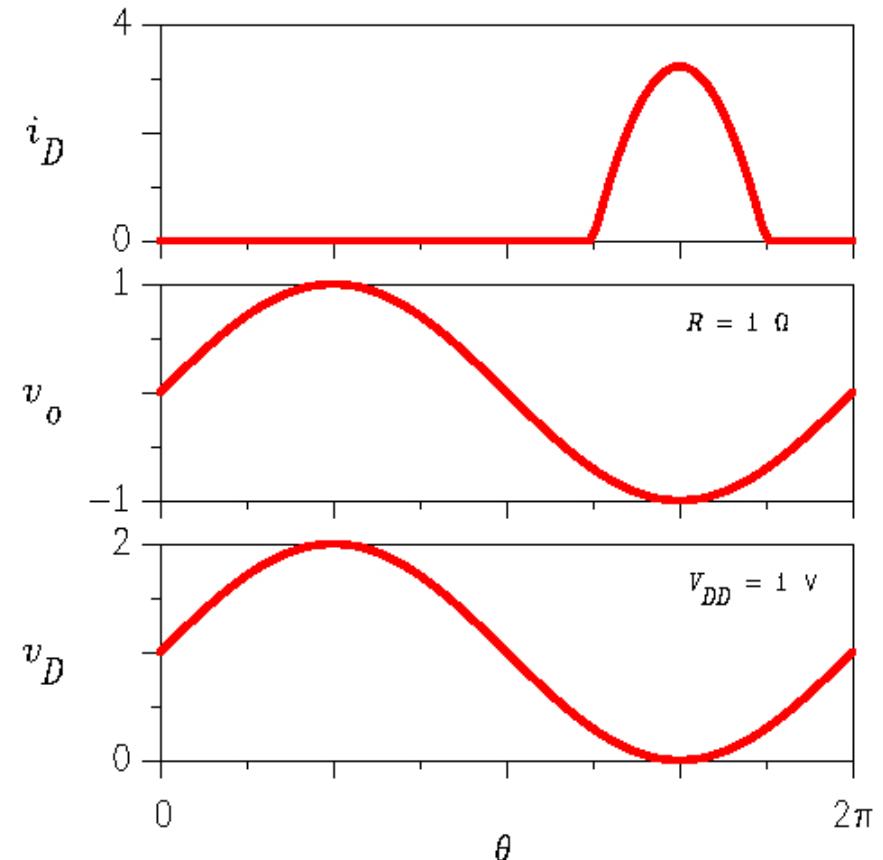


- Drain current $< 180^\circ$
- Increased efficiency
- Inherent harmonics and nonlinearity

BIAS - CLASSES A, B, AND C

EFFICIENCY

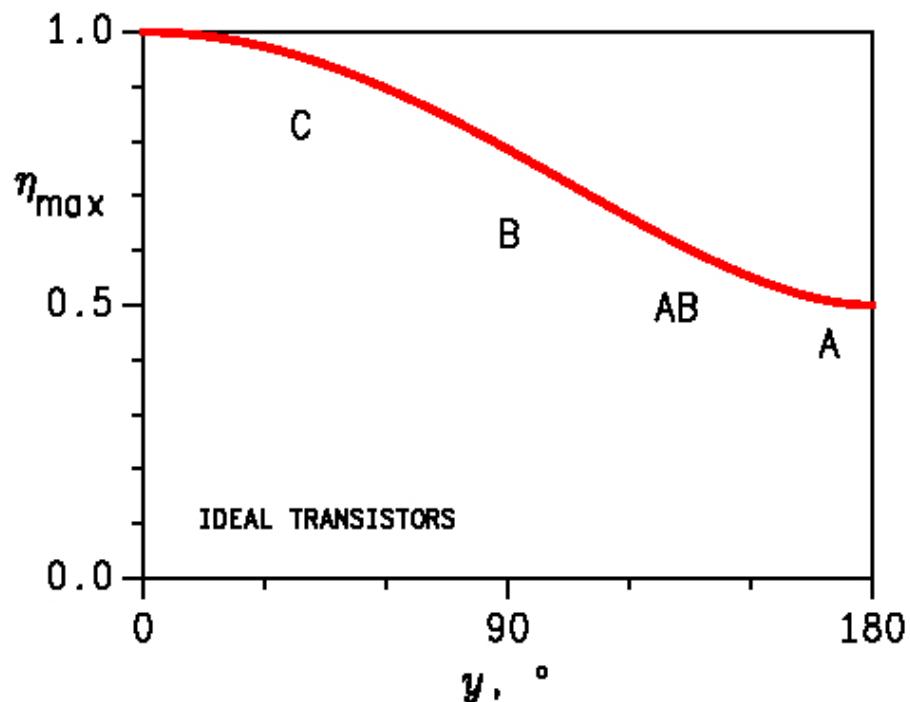

POWER CAPABILITY

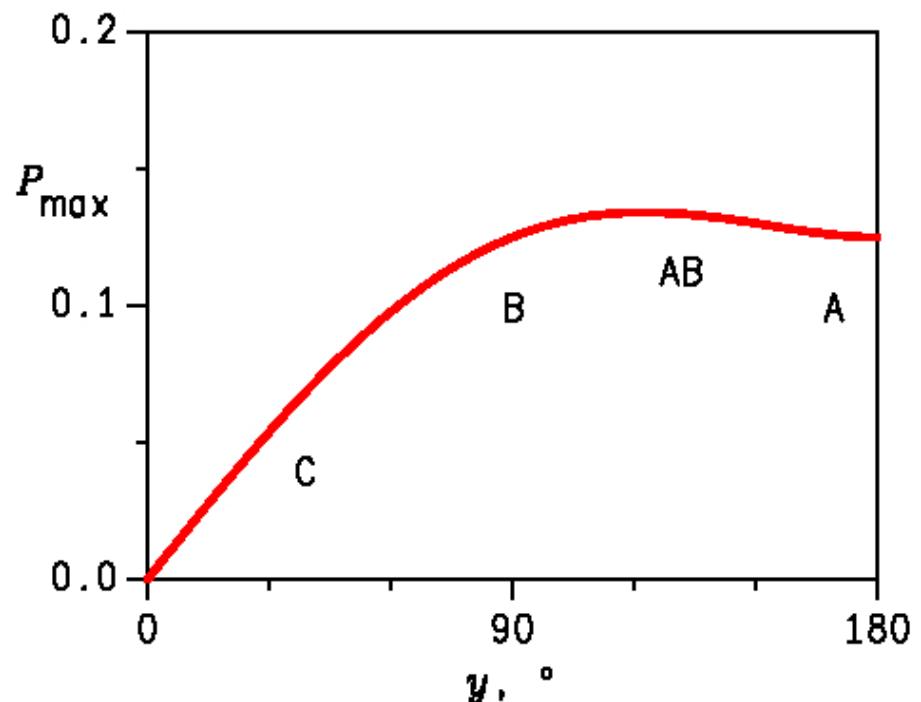

Gate bias controls conduction angle

360°: Class A - linear


245°: Class AB - maximum power

180°: Class B - linear

<180°: Class C


CLASS-D POWER AMPLIFIER

CIRCUIT

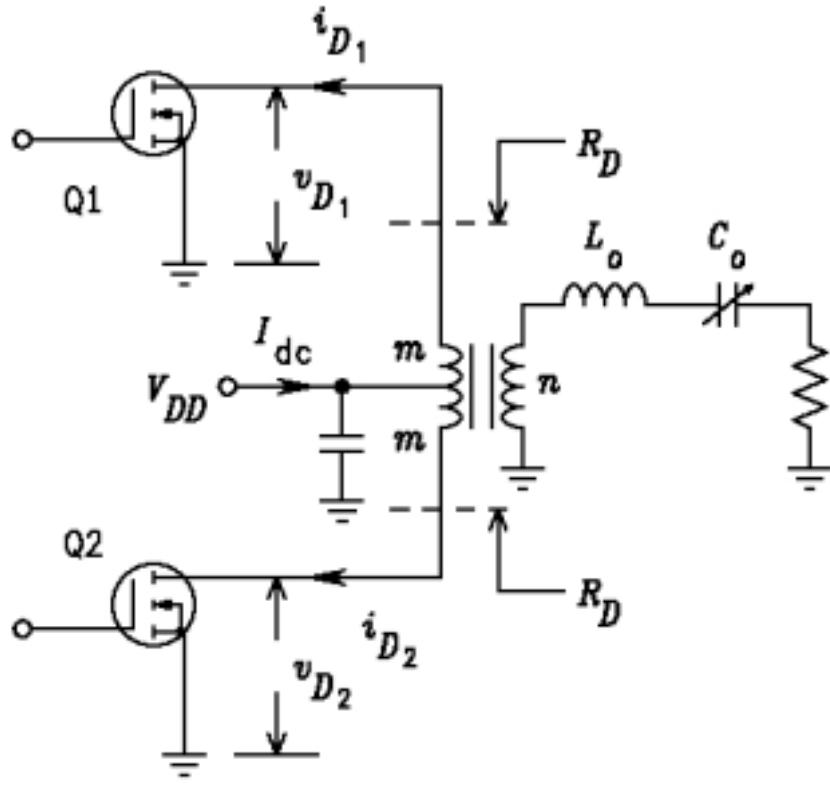

- $R_D = (m/n)^2 R_o$
 - Q1 and Q2 on/off alternately
 - $\approx 180^\circ$ conduction angle

WAVEFORMS

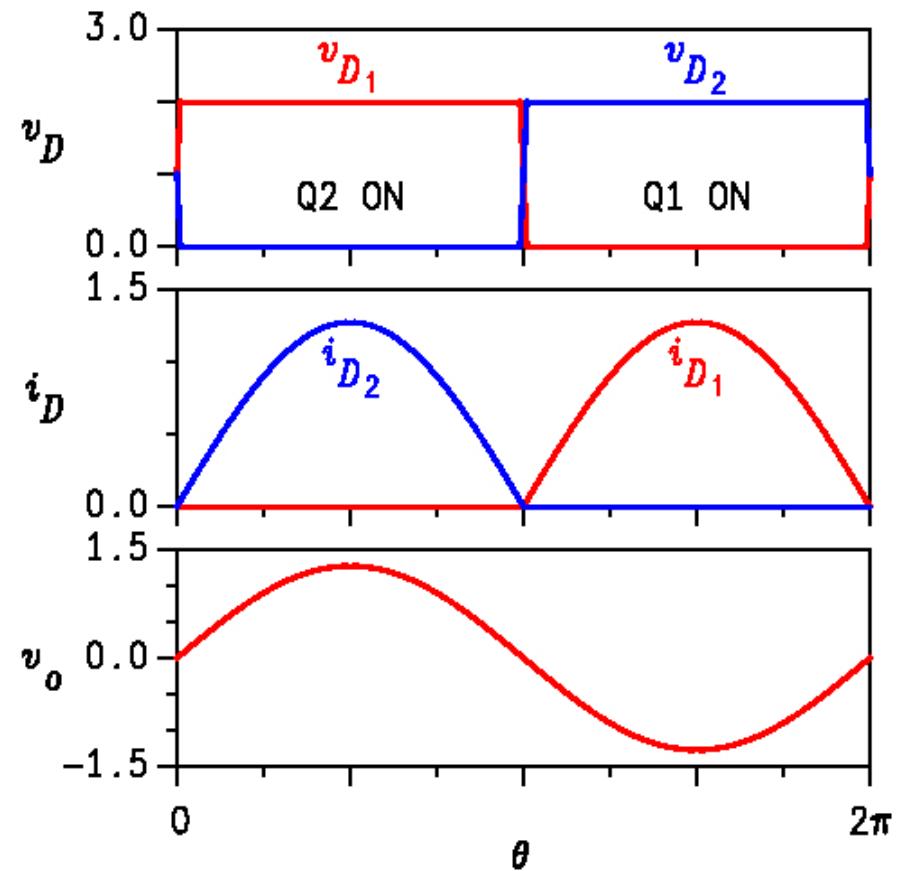


$$\eta = 1 \quad P_{\max} = 0.318$$




CLASS D - CURRENT SWITCHING

CIRCUIT

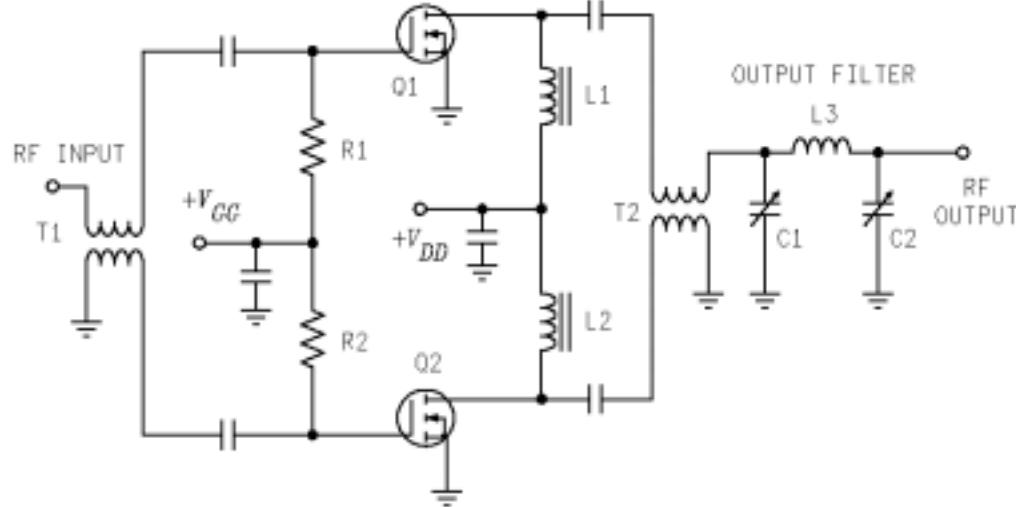

WAVEFORMS

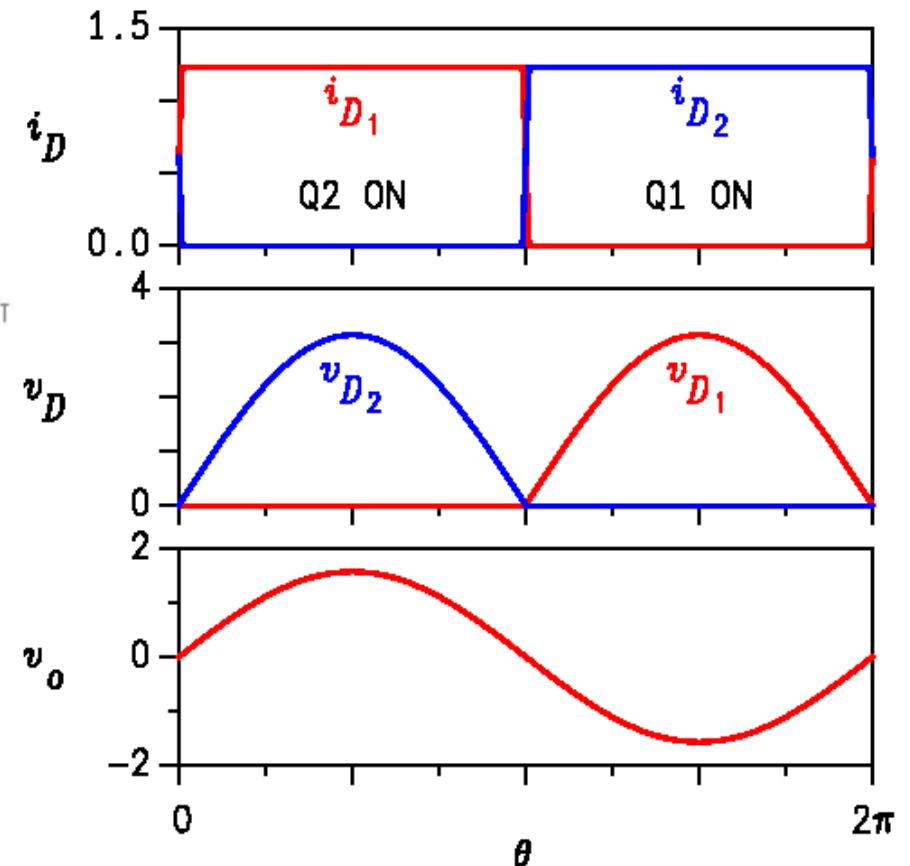

- $R_D = (m/n)^2 R_o$
- Q1 and Q2 on/off alternately
- $\approx 180^\circ$ conduction angle

$$\eta = 1 \quad P_{\max} = 0.318$$

CLASS D - CHARACTERISTICS

LOSSES

- On-state resistance
- Switching time
- Drain capacitance

TYPICAL USES

- Voltage switching: LF/MF/HF PAs
- Current switching: 1 GHz

ADVANTAGES

- Maximum power for FET ratings
- Easy to tune

DISADVANTAGES

- Capacitive loss increases with frequency
- Timing errors create short circuit
- Soft drive usually needed

CLASS D - PROTOTYPES

HF

VHF/UHF

VMOS FETs

1.8 - 30 MHz

300 - 400 W

70 - 80%

GaN HEMTs

25 - 400 MHz


70 - 100 W

60 - 70%




CLASS-E POWER AMPLIFIER

CIRCUIT

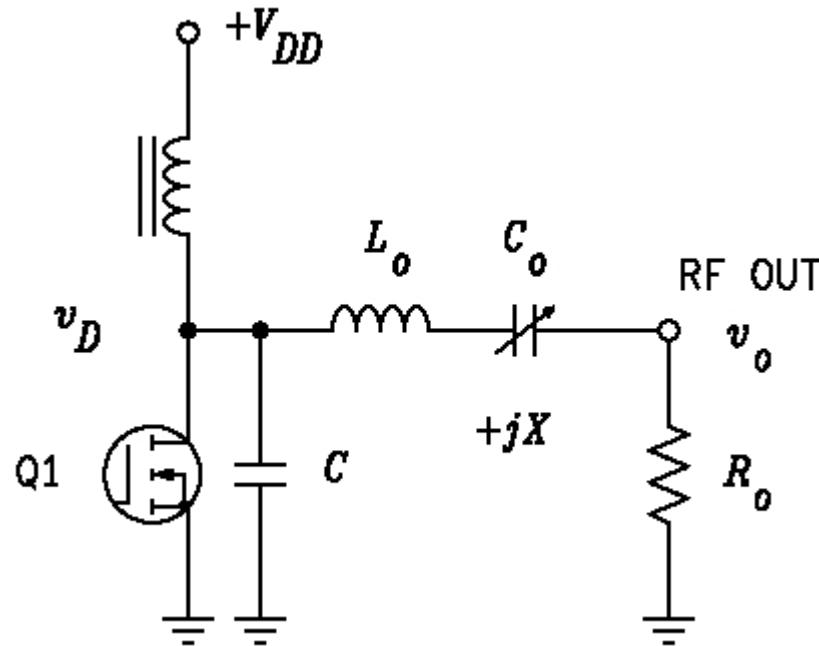

WAVEFORMS

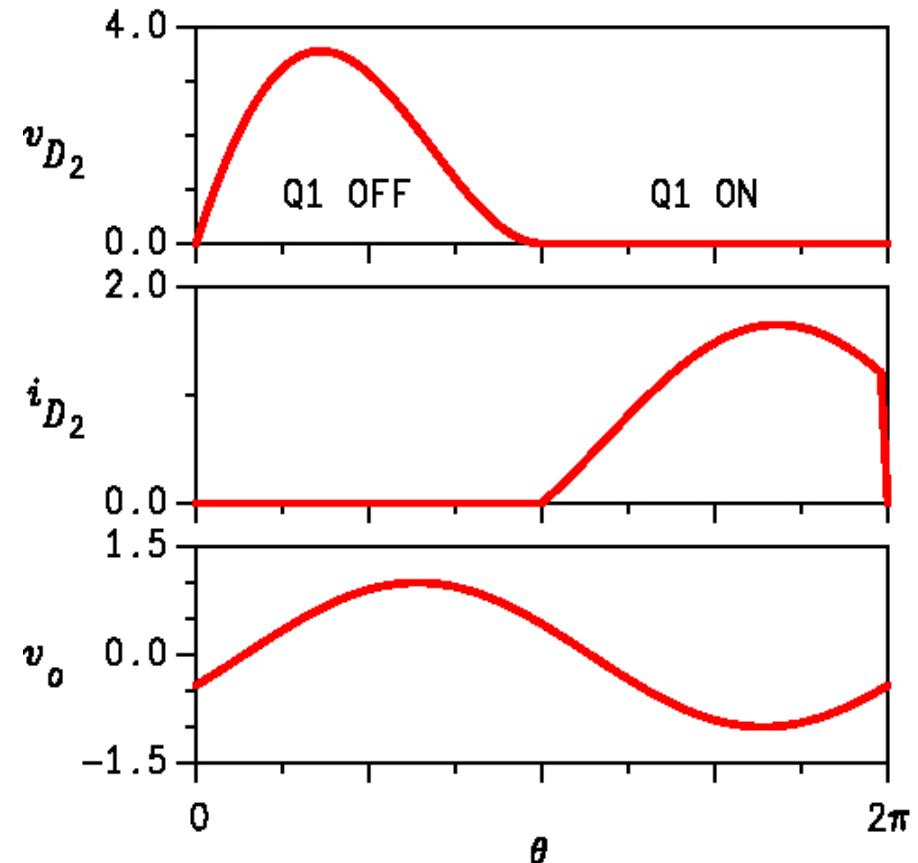

- Transistor = switch
- Dynamics \rightarrow waveform
- Discharge C_{DS}
- $\eta = 1$

$$P_{\max} = 0.098$$

CLASS E - CHARACTERISTICS

LOSSES

- On-state resistance
- Switching time

TYPICAL USES

- VHF/UHF PAs (true transient class E)
- HF PAs using "low-cost" MOSFETs
- Microwave PAs
(transmission-line approximations)

ADVANTAGES

- No loss from drain capacitance
- No short from timing error

DISADVANTAGES

- Lower output than class D
- Higher loss from R_{on}

CLASS E - PROTOTYPES

HF/VHF

VHF/UHF

VMOS FET

1.8 - 128 MHz

200 W

70 - 90%

LDMOS FET

25 - 400 MHz


60 - 78 W

60 - 80%




CLASS-F POWER AMPLIFIER

CIRCUIT

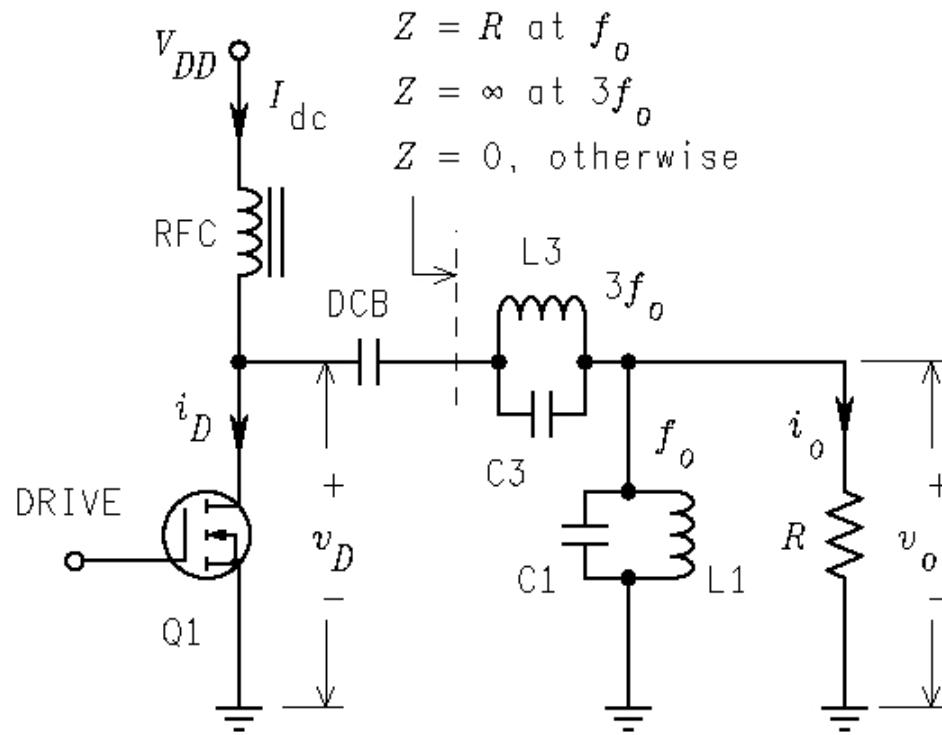


WAVEFORMS

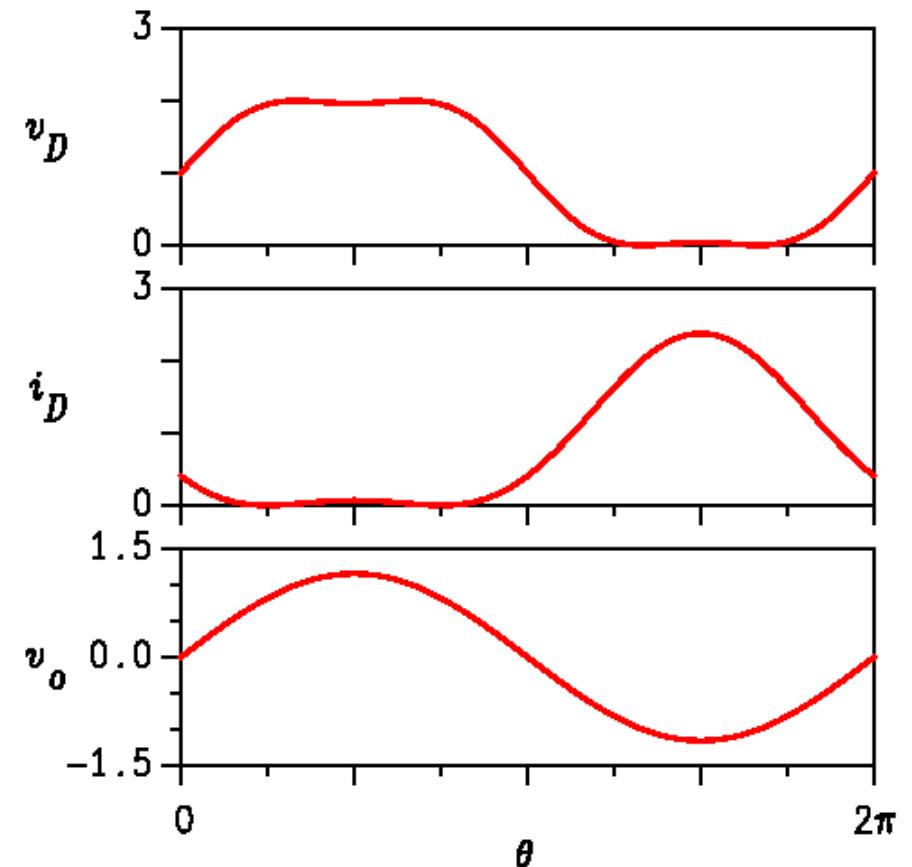


- Voltage \approx square wave
- Current \approx half sine wave
- Power and efficiency increased

CLASS-F - ALL HARMONICS

CIRCUIT

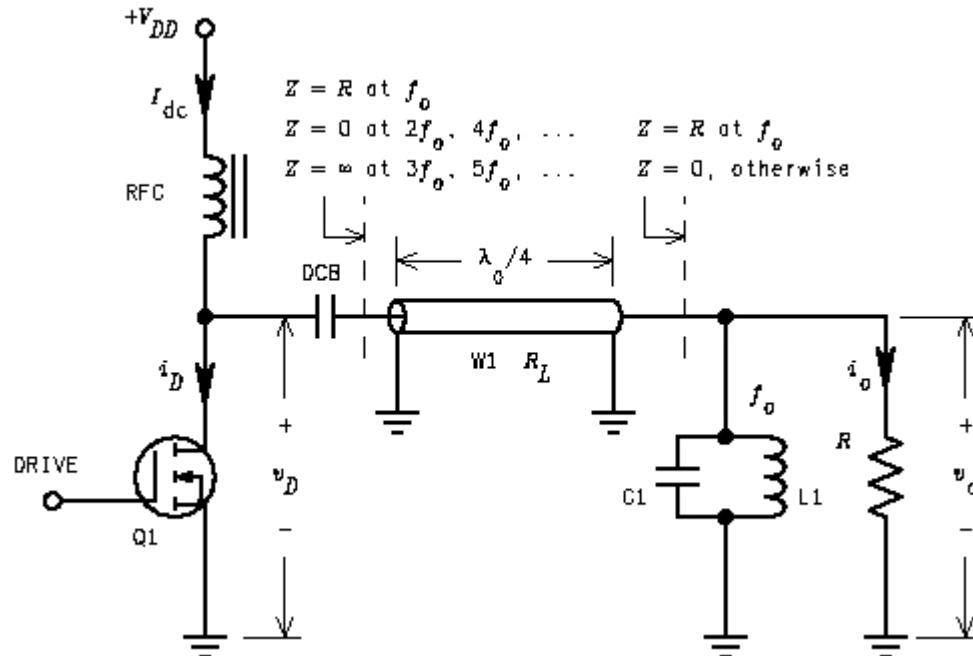

WAVEFORMS

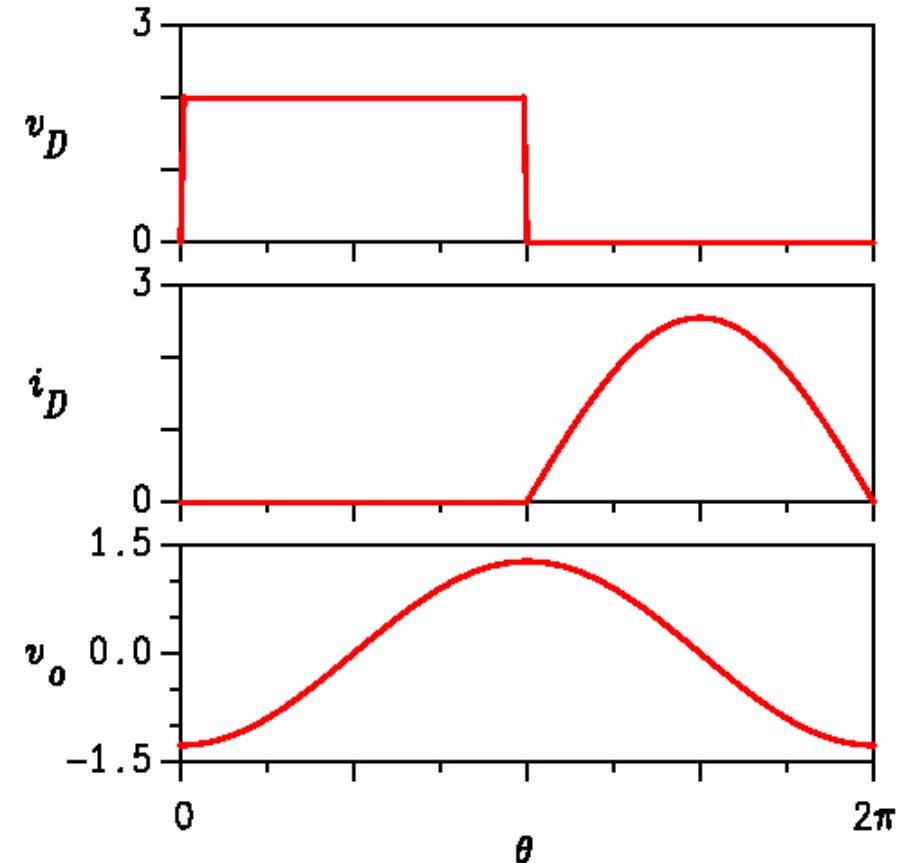


- Quarter-wavelength T line
- Voltage = square wave
- Current = half sine wave
- Half of class-D PA


$$\eta = 1 \quad P_{\max} = 0.159$$

CLASS-F - CHARACTERISTICS

EFFICIENCY

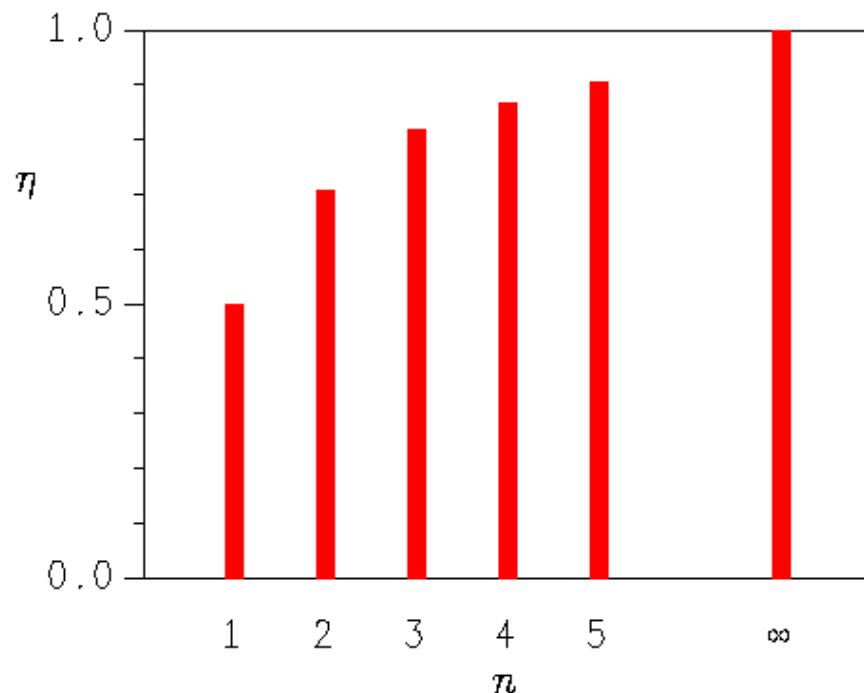


POWER OUTPUT

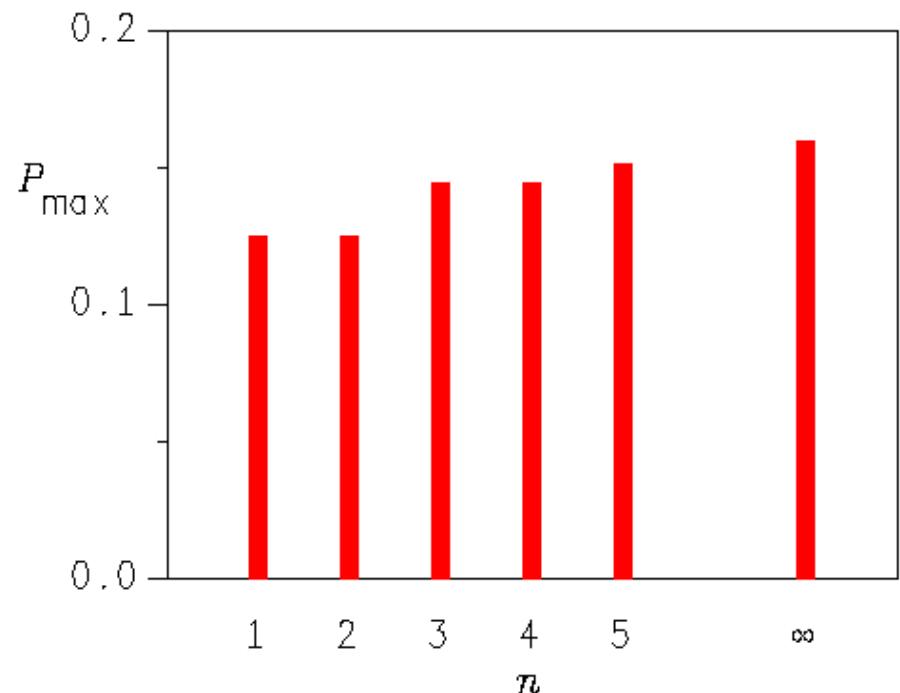

- Efficiency and output increase with number of controlled harmonics
- Progressively smaller increases
- Evens and odds affect efficiency
- Odds affect output
- Can (must) tune-out drain capacitance
- Transmission-line resonators
- Good for UHF, microwave

CLASS-F – MICROWAVE

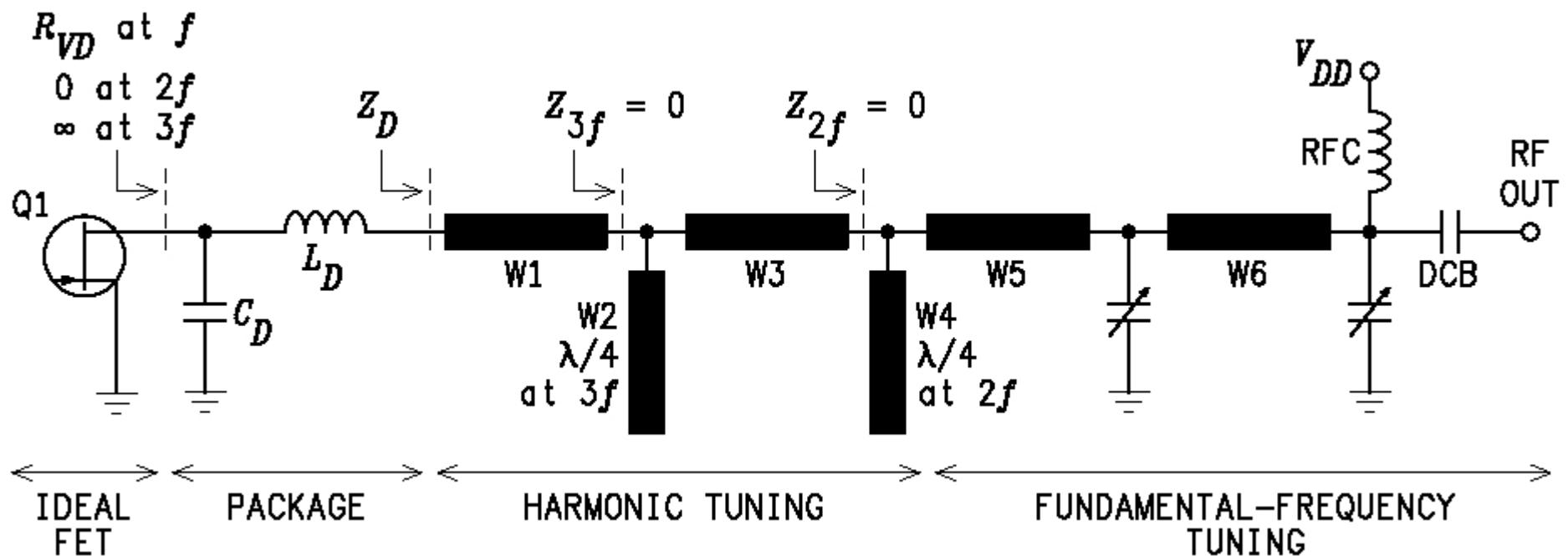

- Virtual drain of ideal FET sees ideal impedances
- $3f$ and $2f$ shorts by $\lambda/4$ lines
- $3f$ short transforms through W1 and package to virtual drain
- Circuit to right does not affect $3f$
- $2f$ short transforms through W3, W2, W1, package to virtual drain
- Circuit to right does not affect $2f$
- Remaining components match fundamental

CLASS F - PROTOTYPES

500 MHz

1.2 GHz

GaN HEMT

54 W

71%


GaN HEMT

55 W


74%

MICROWAVE CLASS E vs. CLASS F

CLASS E

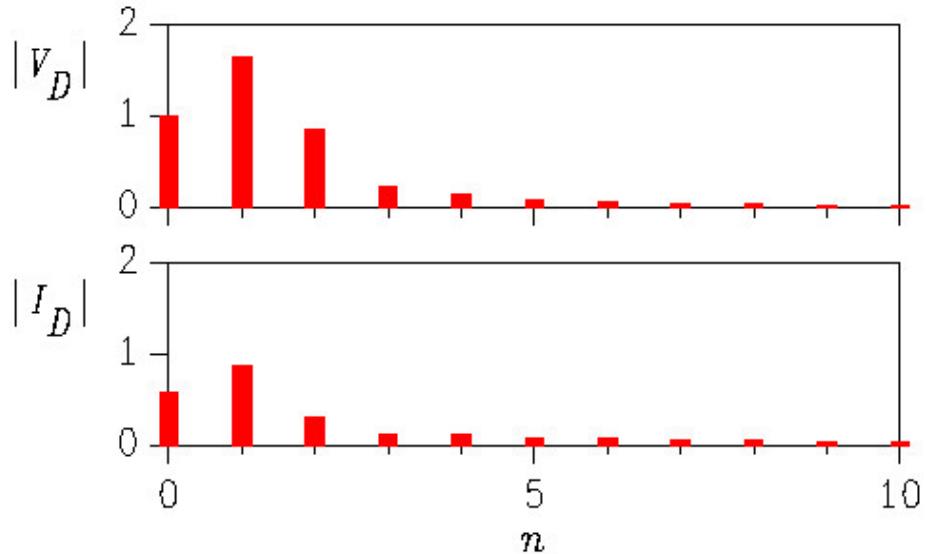

CLASS F

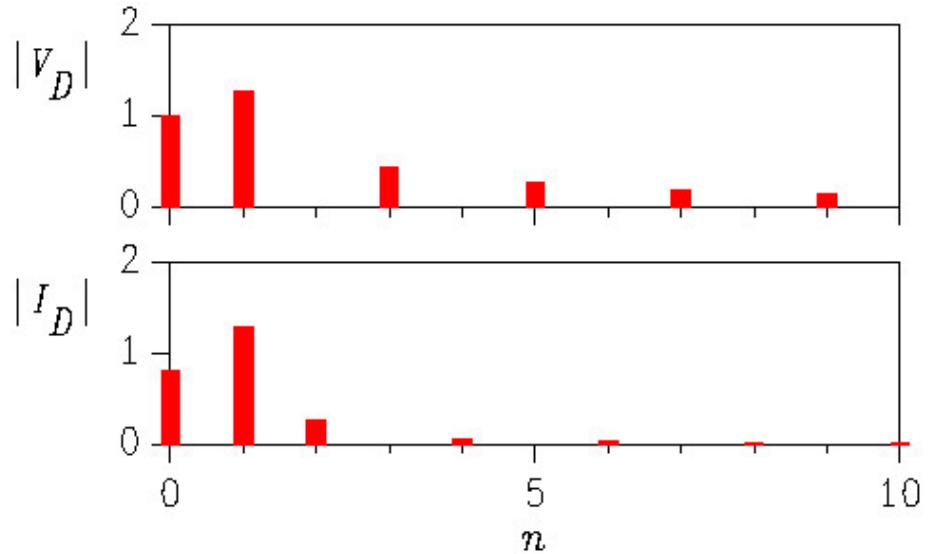

FUNDAMENTAL

$R + jX (\approx 45^\circ)$


R

HARMONICS


V and I : Nonzero
 90°
No power

$V > 0, I = 0$ or
 $V = 0, I > 0$
No power

CLASS C, E, AND F - FINITE HARMONICS

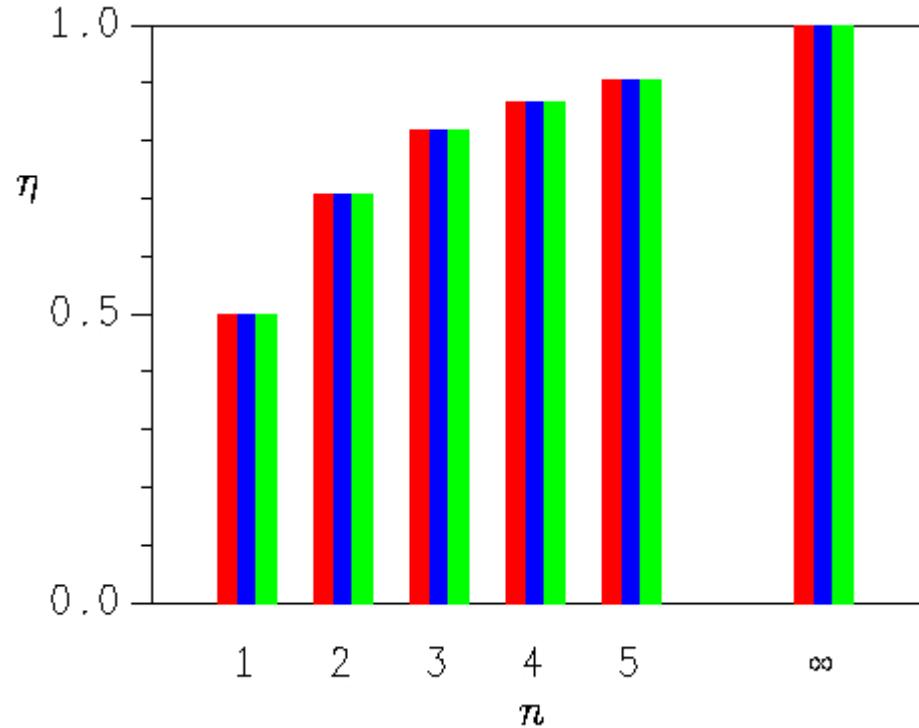

Depends upon n
Independent of class

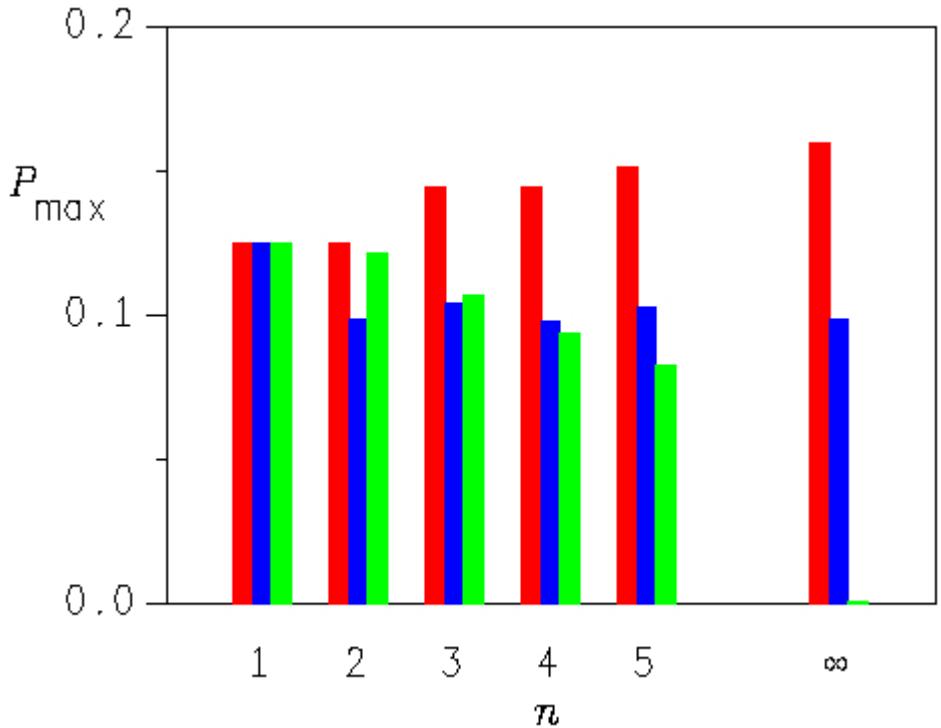

Highest for F
Class C: Decreases with n

REAL UHF/MICROWAVE HEPAS

REALITY

- FET not ideal switch
- FET not ideal current source
- Varactor drain capacitance
- Harmonics happen

CLASS EF

- T-line network like class F
- Resonators control $2f$ and $3f$
- Drain capacitance for higher f
- Soft switching
- Small inductive reactance at f
- Power output of class F
- Efficiency of class E

TRANSMISSION-LINE CLASS E

- Finite-harmonic approximation
- T-line network like class F
- f : $R + jX (\approx 45^\circ)$
- $2f$: \approx ideal
- Both v_D and i_D have f and $2f$

CLASS J

- Cripps terminology
- v_D : 2 harmonics
- i_D : Half sine wave
- f : $R + jX (\approx 45^\circ)$
- nf : Drain capacitance
- $\eta = 0.785$
- $P_{\max} = 0.0858$





ARCHITECTURES - TWO CATEGORIES

1. HIGH EFFICIENCY OVER
MODULATION ENVELOPE


2. HIGH EFFICIENCY
OVER DYNAMIC RANGE

PREDISTORTION

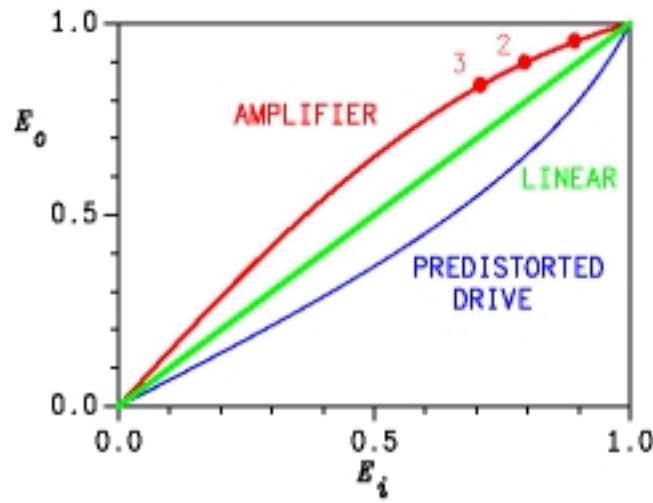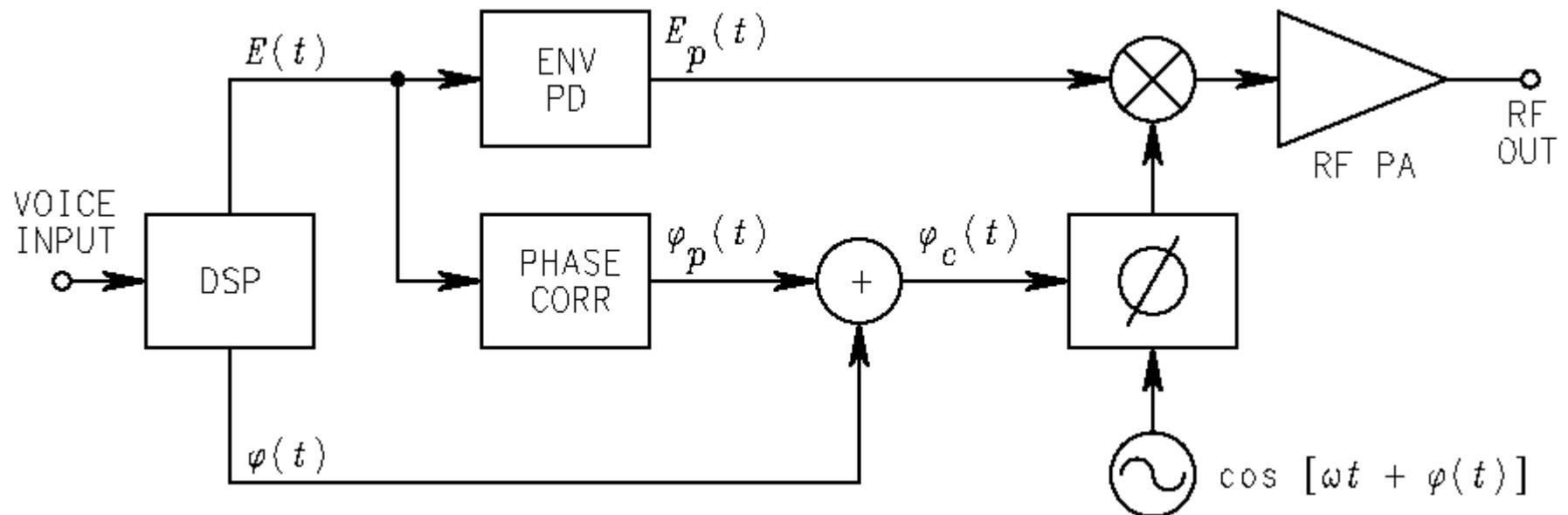

Nonlinearity



- Backoff
- Reduced η

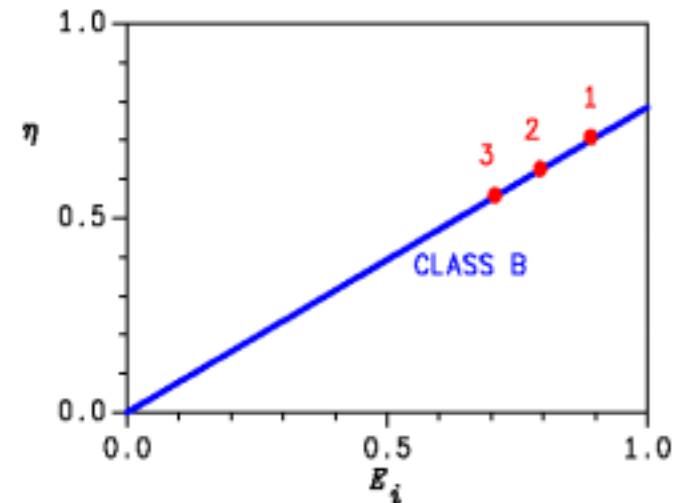

Predistortion

- Eliminates nonlinearity
- PEP efficiency


KAHN TECHNIQUE

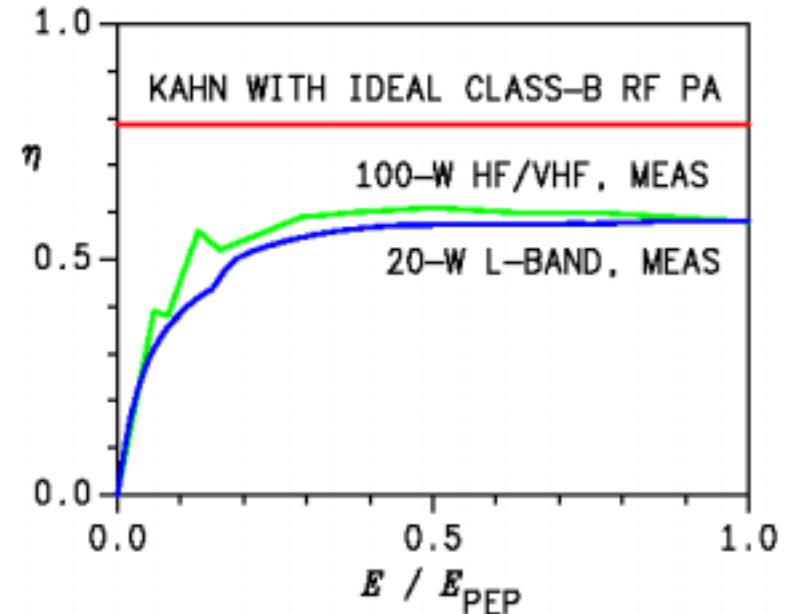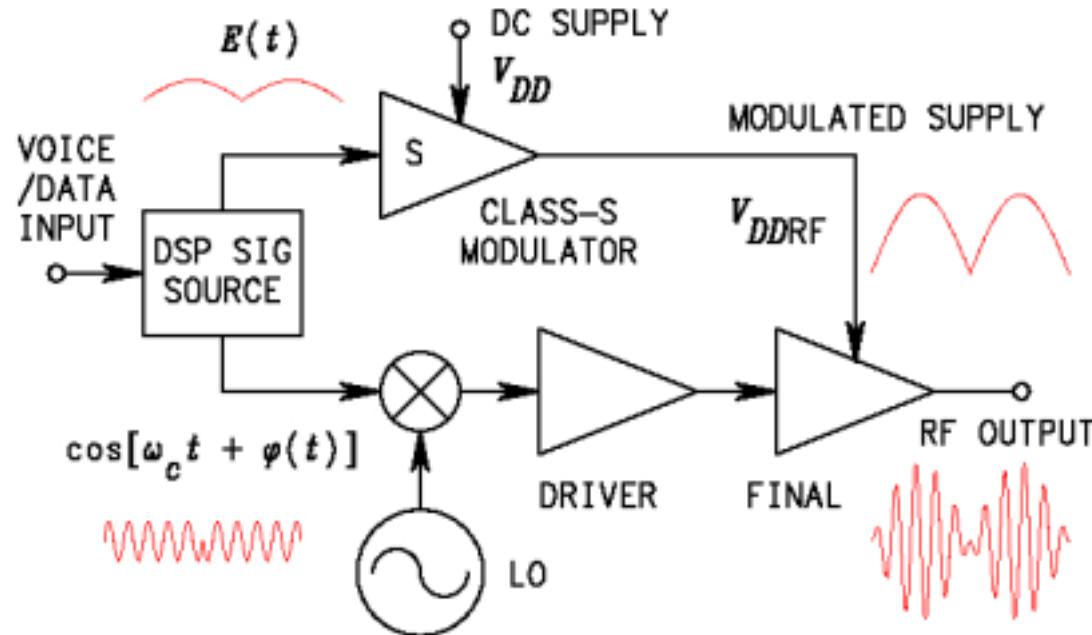


- High-efficiency linear transmitter
- RF signal: Simultaneous AM, ΦM
- Saturated RF PA
- High-level AM
- Average efficiency 3 to 5 times class B

MODULATORS FOR KAHN TECHNIQUE

CLASS S

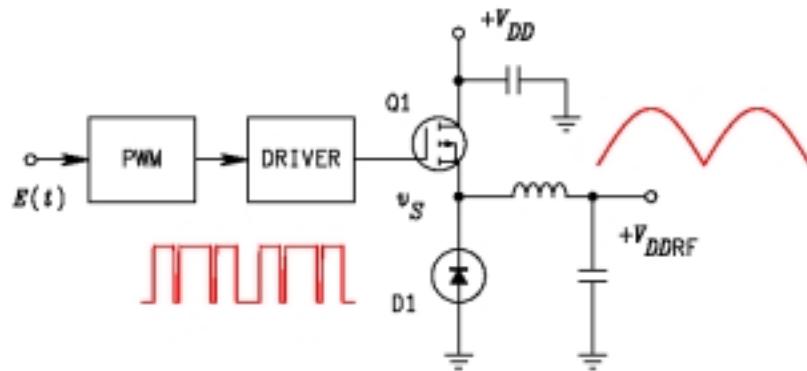

SPLIT BAND

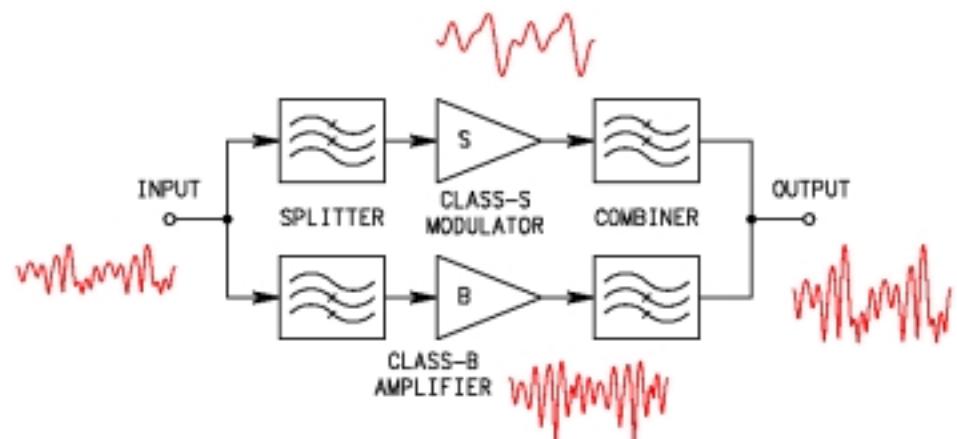

- Q1-D1 = SPDT switch
- Efficiency > 90%
- Wide dynamic range
- $f_s > 6-7 B_{RF}$

LF COMPONENTS

- Most of power
- Amplify efficiently – class S

HF COMPONENTS

- Amplify linearly – class B

U.S. patent 6,252,634

PROTOTYPE KAHN TRANSMITTERS

HF-VHF

L BAND

MRI

10 - 128 MHz

500-kHz bandwidth

Predistortion

200 W PEP

70-80%

2x average efficiency

Radar

1.2 GHz

500-kHz bandwidth

Predistortion



50 W PEP

60%

2x average efficiency



DOHERTY TRANSMITTER

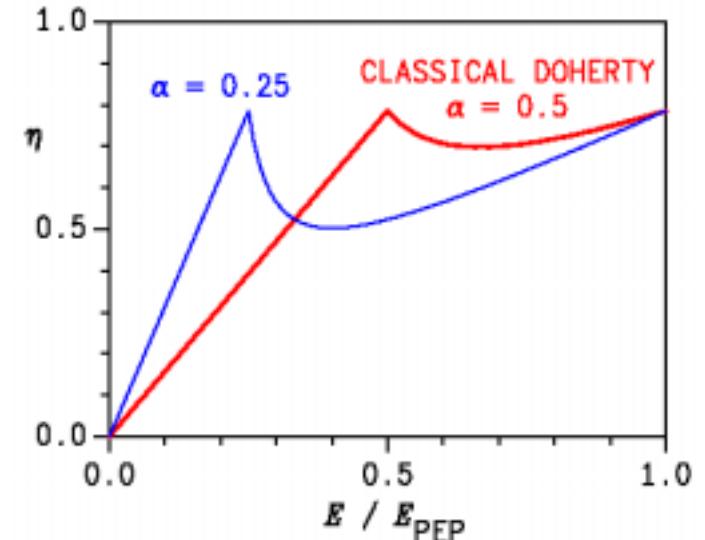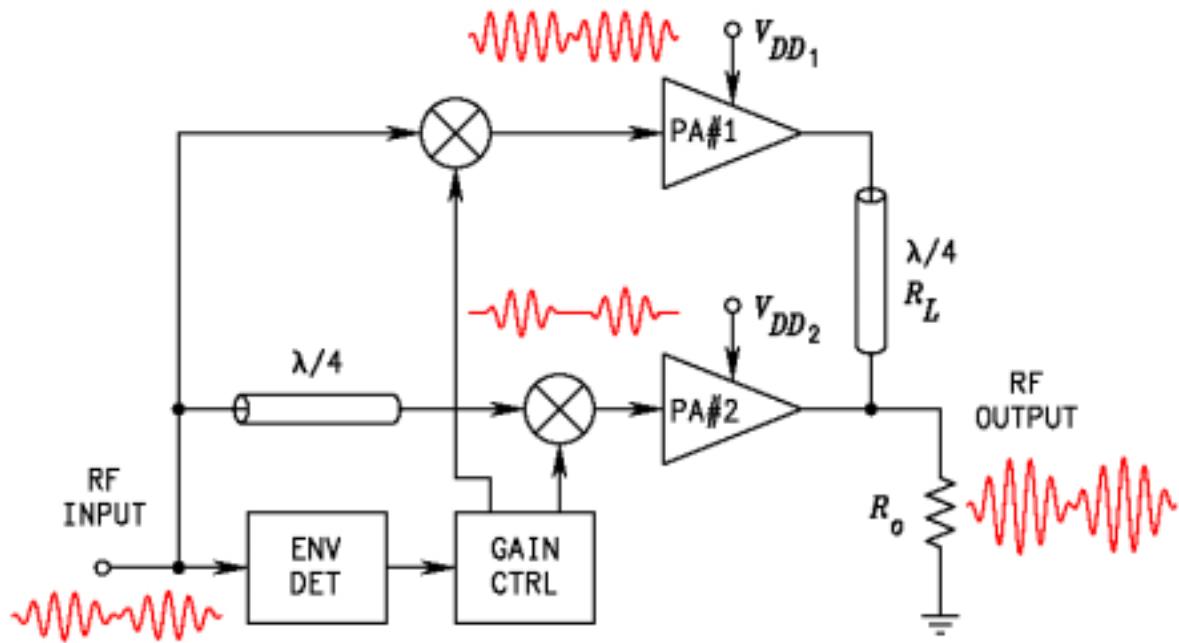

LOW AMPLITUDES



- PA #1 linear
- PA #2 off

HIGH AMPLITUDES

- PA #2 active
- PA #1 saturated

variable load

THREE-STAGE DOHERTY

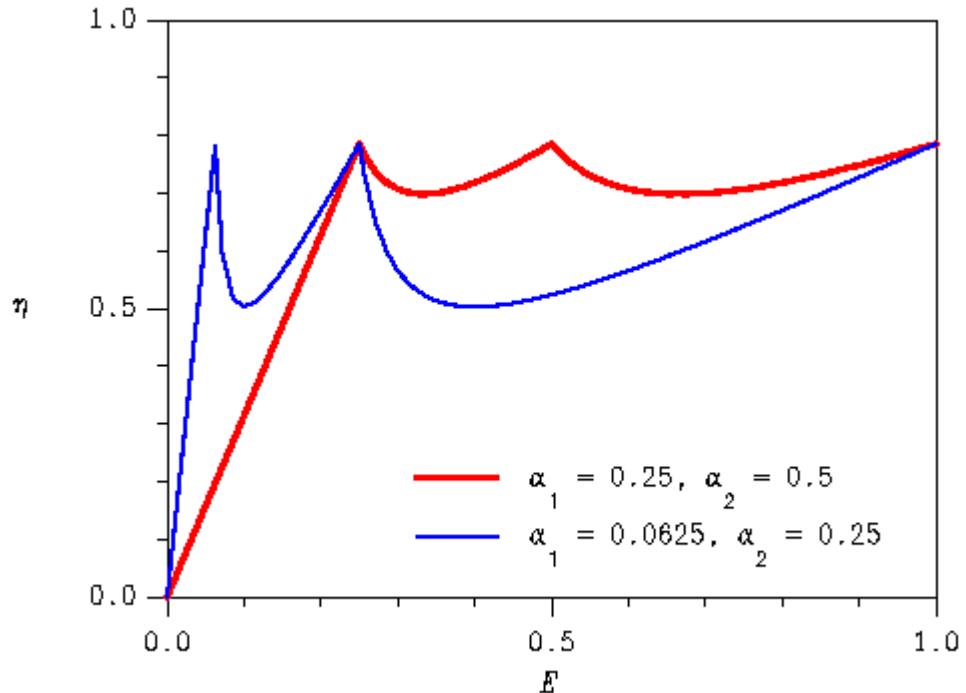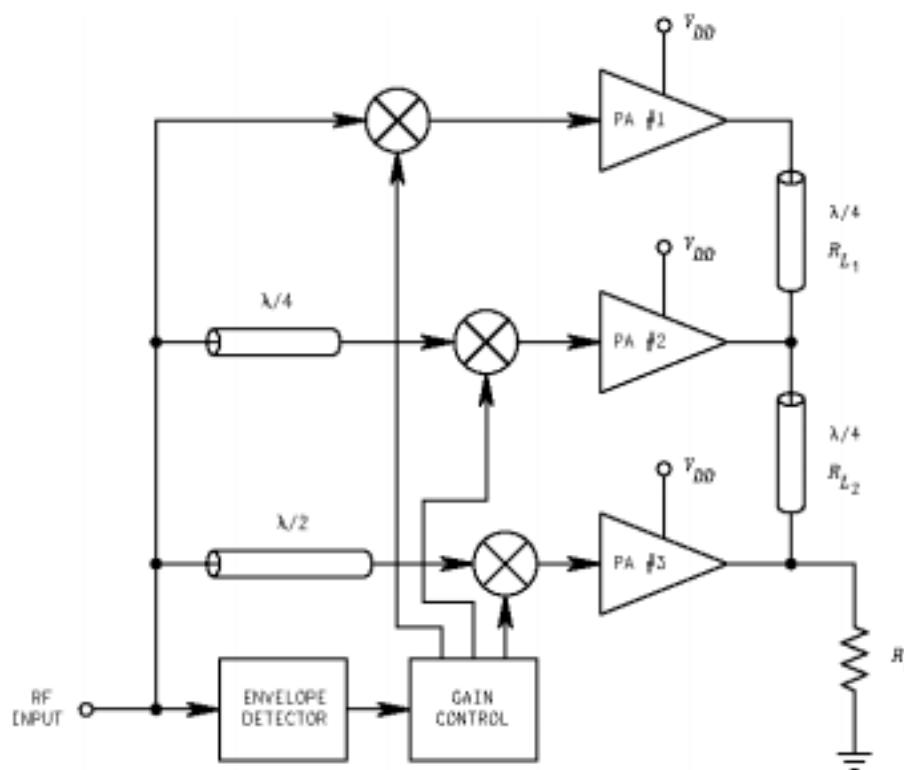

PRINCIPLES

PA1+PA2 = 2-S Doherty at low power

PA1+PA2 = carrier amp at high power

Good efficiency over wide range




AVERAGE EFFICIENCY 10-dB P/A

Class B 28.0 %

2-S Doherty 60.0 %



3-S Doherty 70.0 %

CHIREIX OUTPHASING

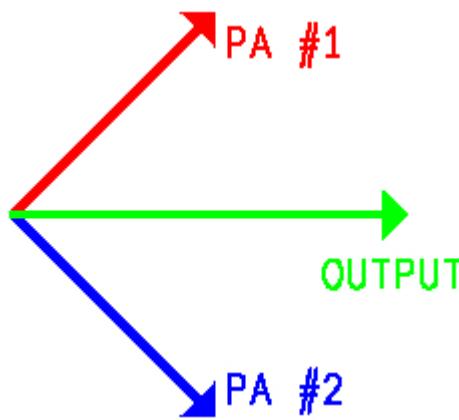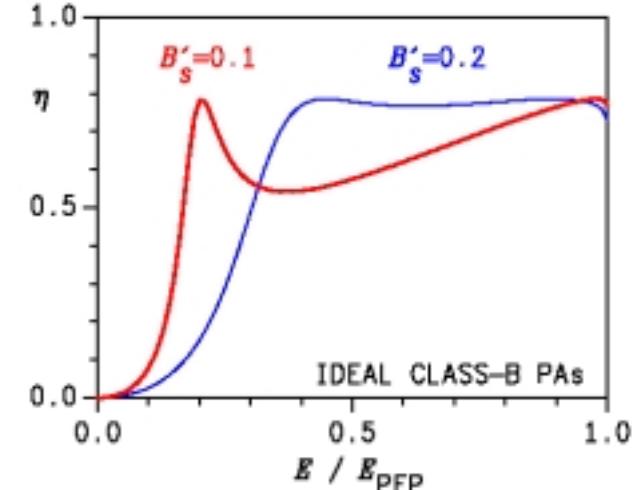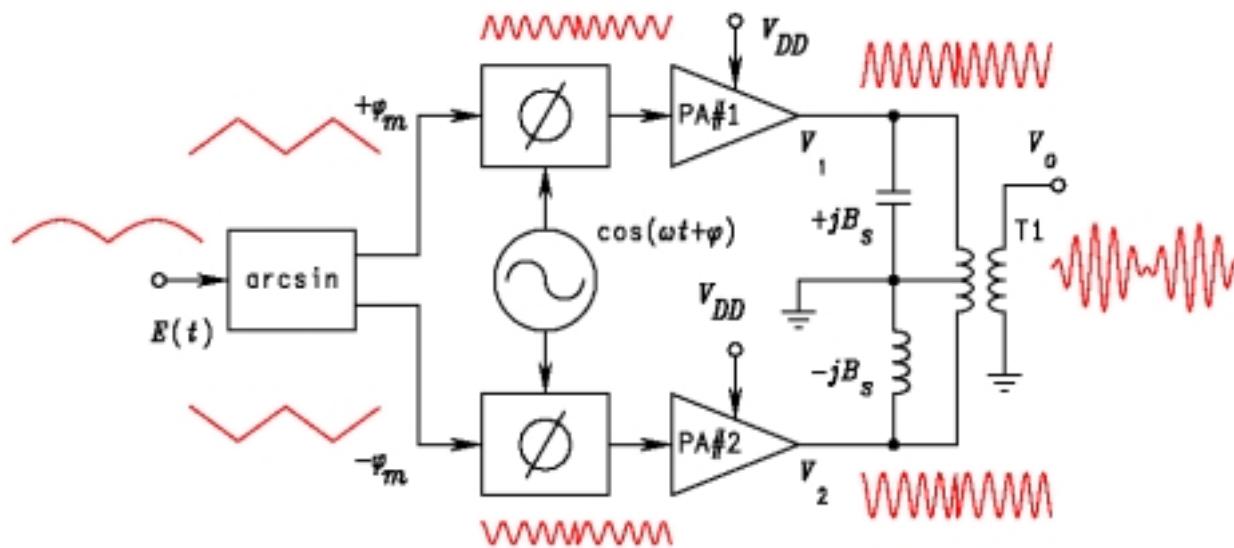



- Vary phases in opposite directions
- PAs saturated
- Sum -> desired amplitude
- Tune-out load reactance mid range
- Wide bandwidth - limited by phase modulator

LOAD MODULATION

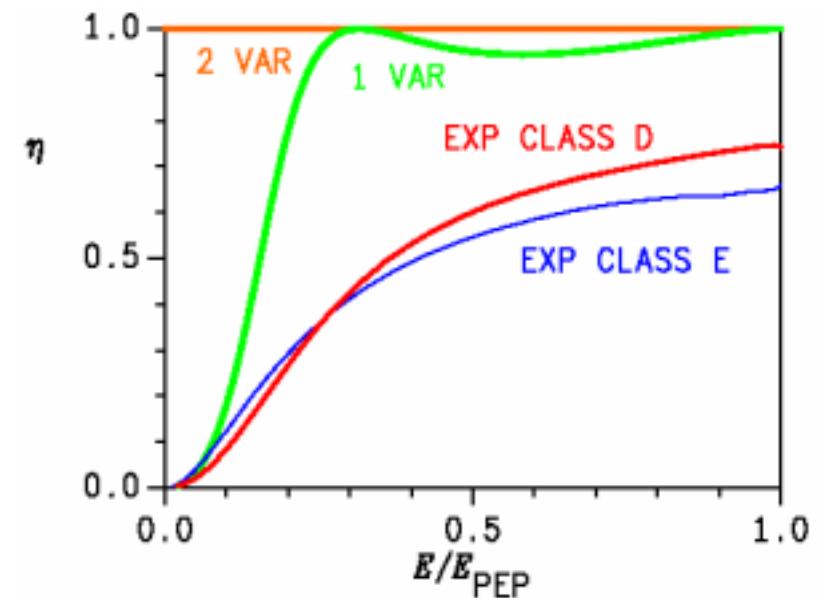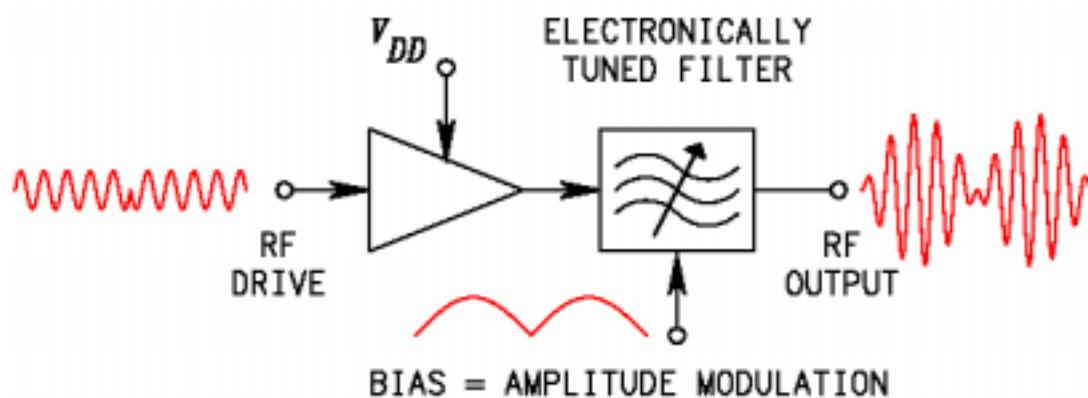

- Vary bias(es) of electronically tuned filter
- Variable load impedance to power amplifier
- Variable output power and amplitude
- Phase information in drive signal
- Wide bandwidth – limited only by bias feed/modulator

PROTOTYPE LOAD-MODULATED PA

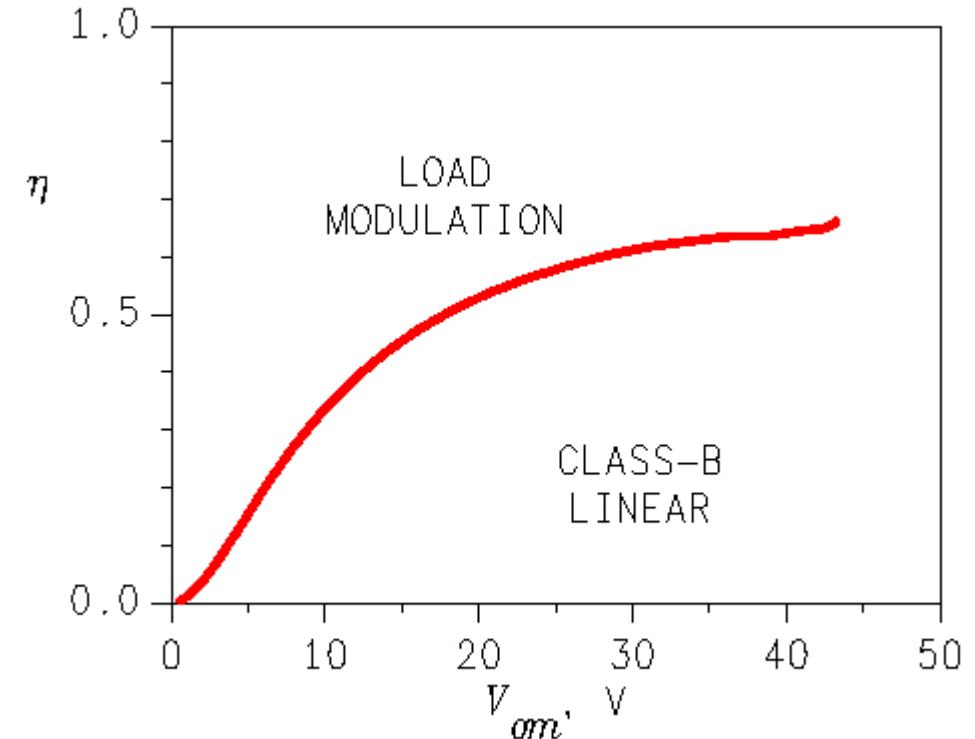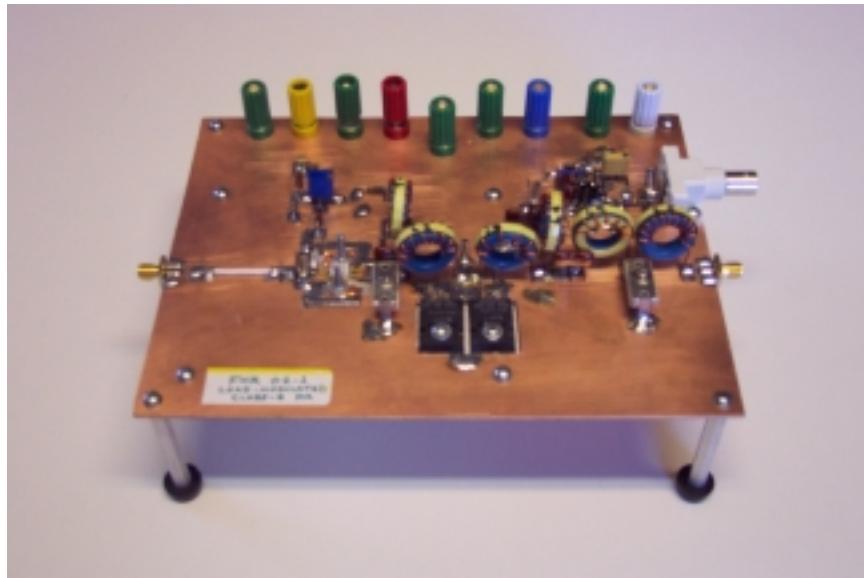

30 MHz

19 W PEP

Varactor = HV MOSFETs

41-dB dynamic range



1 variable element

10-dB peak/average ratio



Average efficiency x2.1

RF PULSE-WIDTH MODULATION

DELTA-SIGMA RF PWM

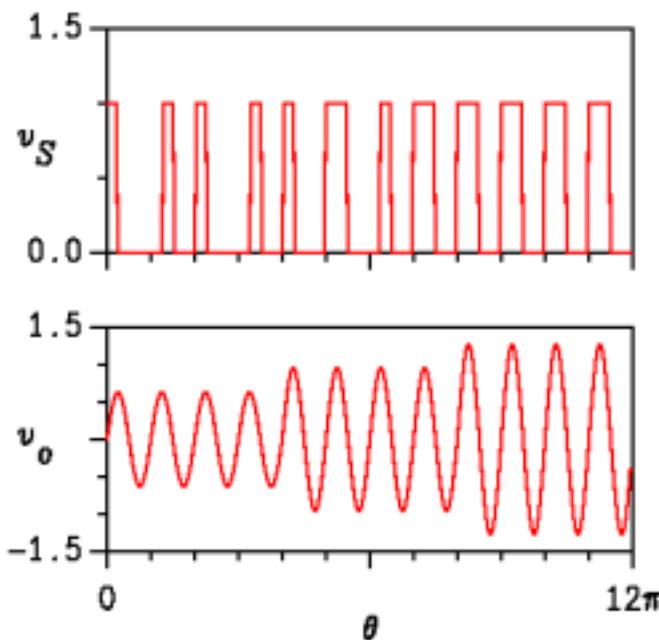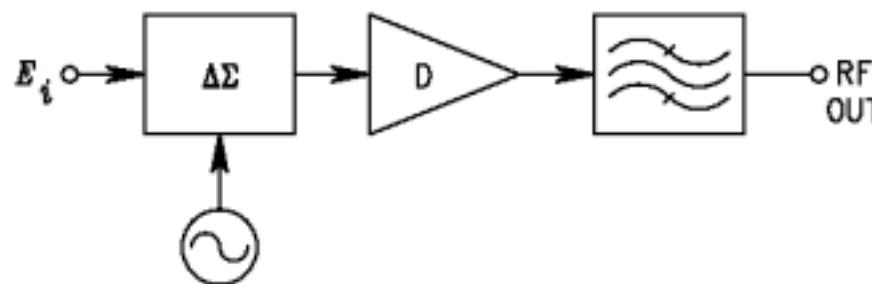

CARRIER PWM

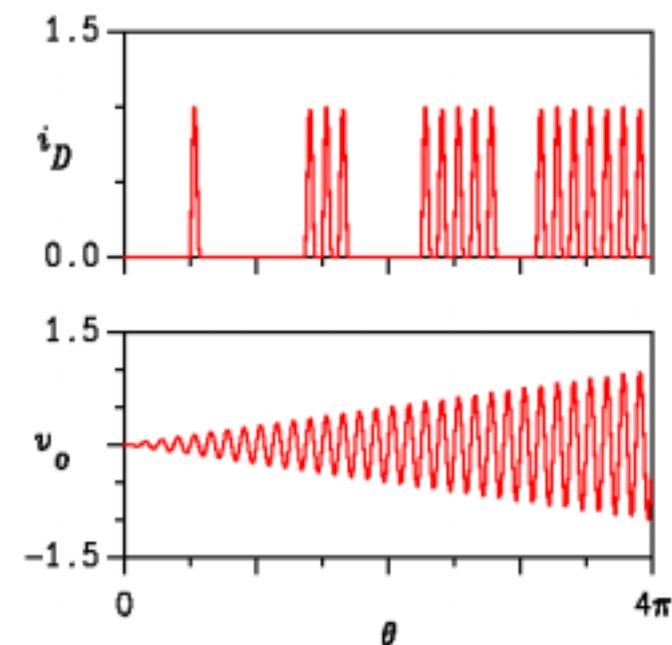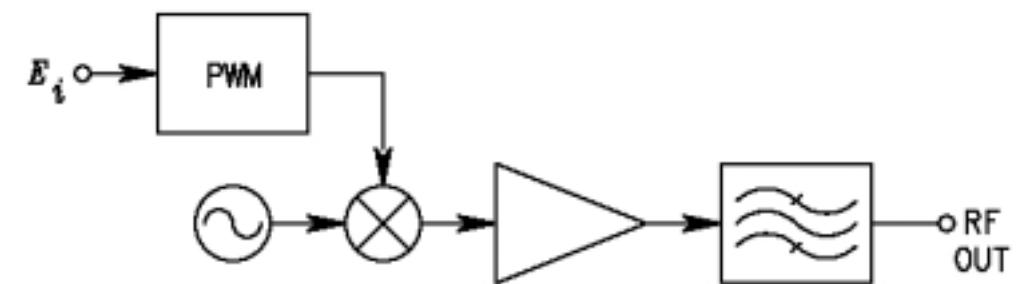

ARCHITECTURES - TWO CATEGORIES

1. HIGH EFFICIENCY OVER
MODULATION ENVELOPE


2. HIGH EFFICIENCY
OVER DYNAMIC RANGE

EFFICIENCY OVER DYNAMIC RANGE


CHARACTERISTICS

- Mobile transmitters
- Wide range of power
- Mostly switched
- Follows PEP,
not envelope

PEP EFFICIENCY (TYPICAL)

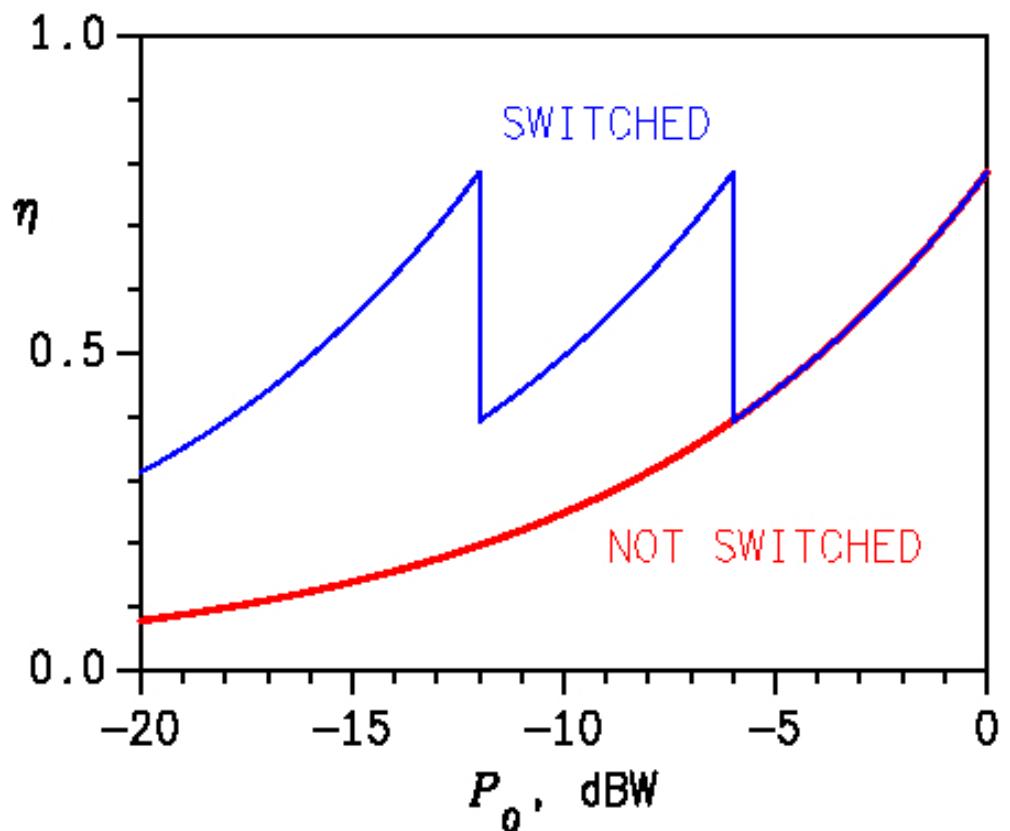


STAGE BYPASSING

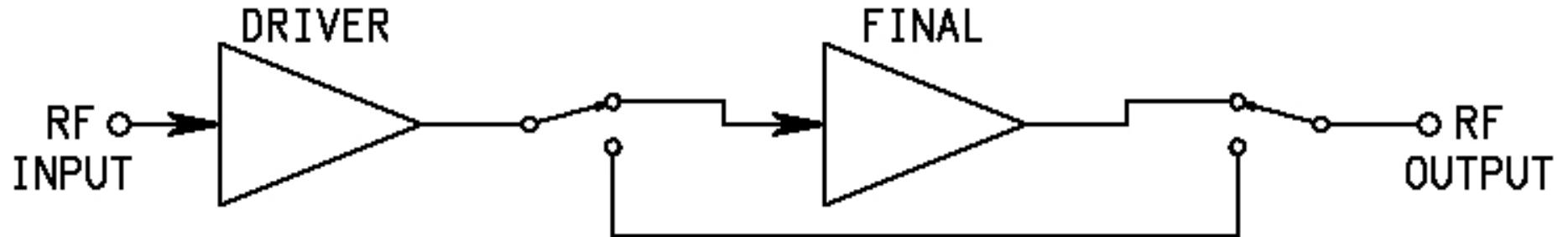


- LOW OUTPUT: Use driver
- HIGH OUTPUT: Use final

ENVELOPE TRACKING - DISCRETE

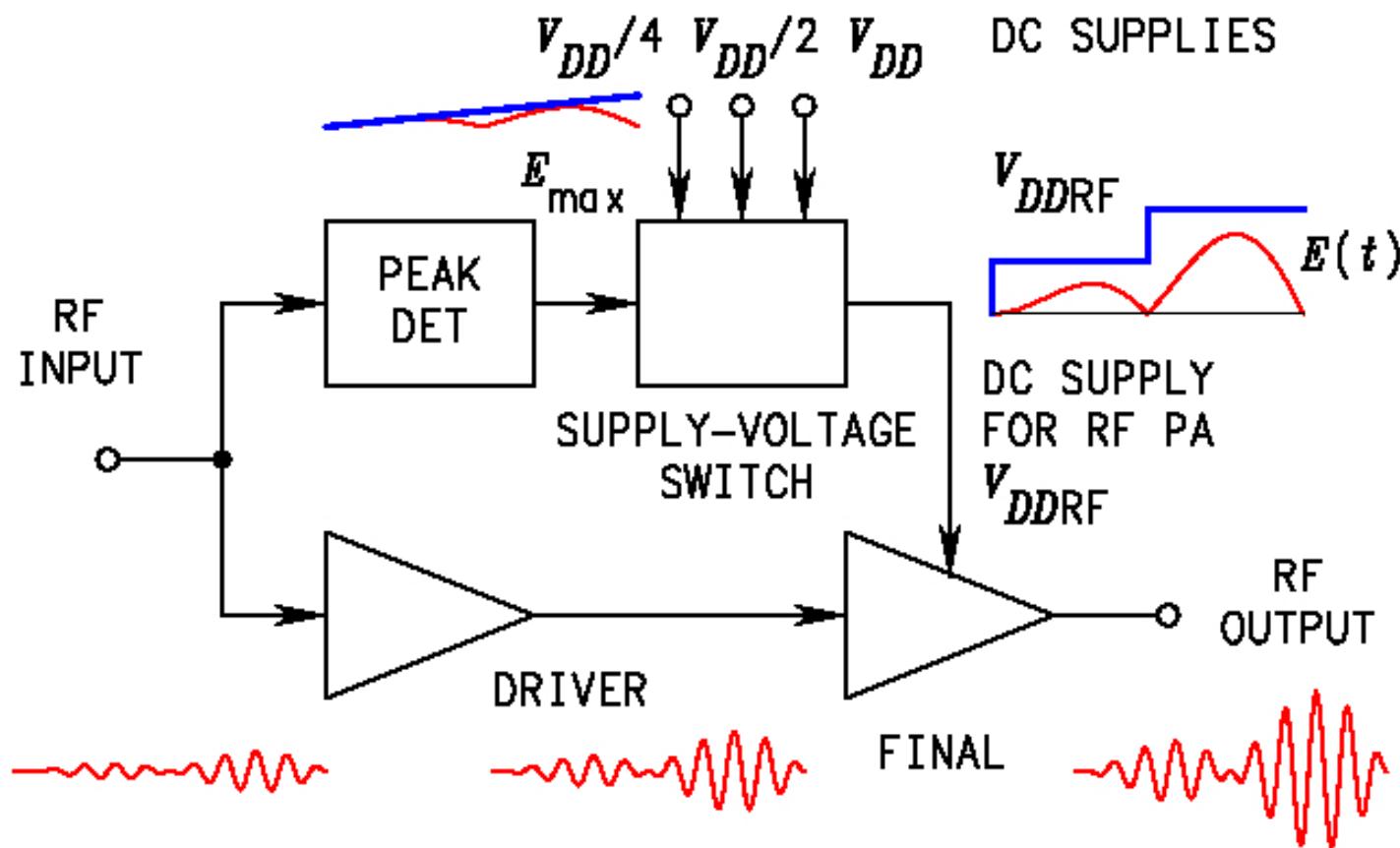


- RF PA: Linear
- Select minimum supply voltage for linear operation
- May cause detuning (mismatch)

ENVELOPE TRACKING - CONTINUOUS

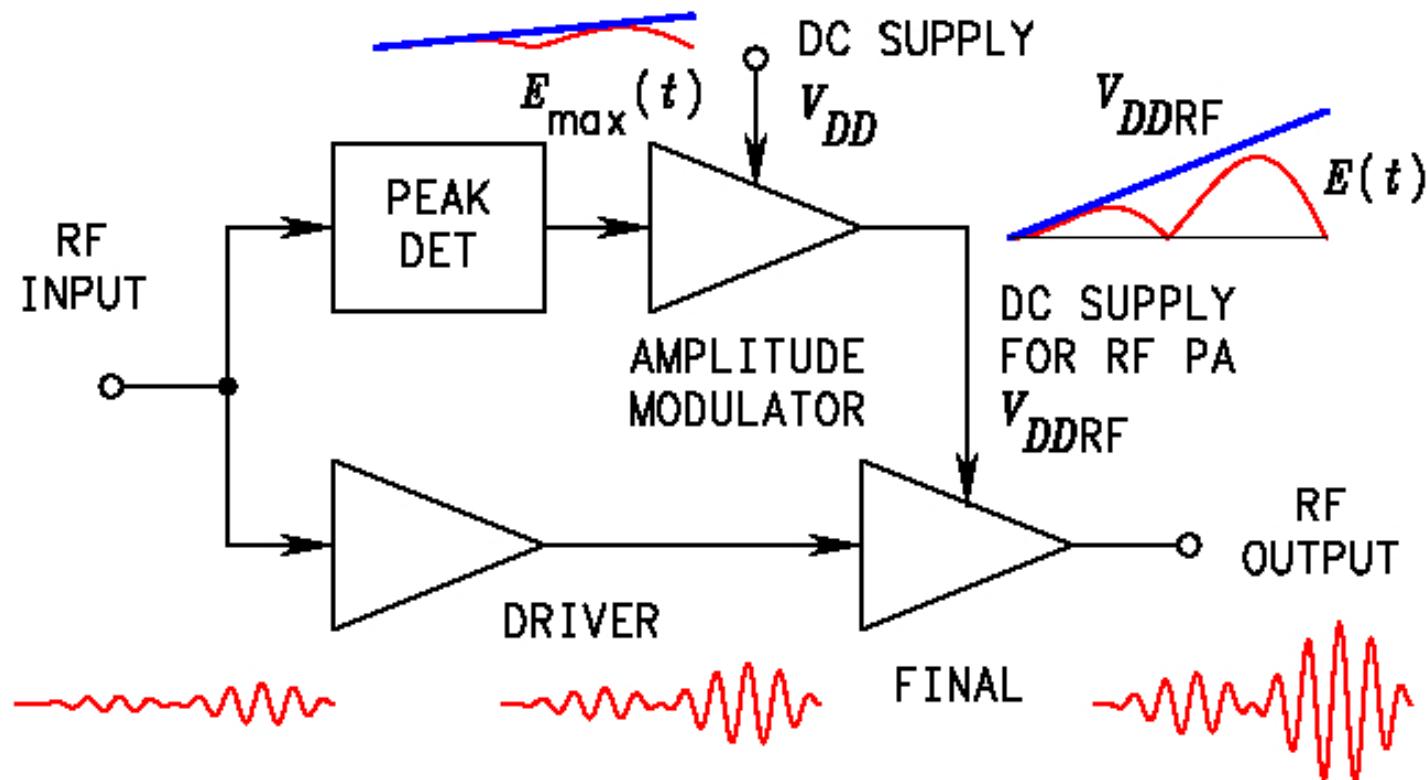


- RF PA: Linear
- Supply voltage = minimum + headroom
- May cause detuning (mismatch)
- Often minimum voltage (boost converter)

LOAD-IMPEDANCE SWITCHING

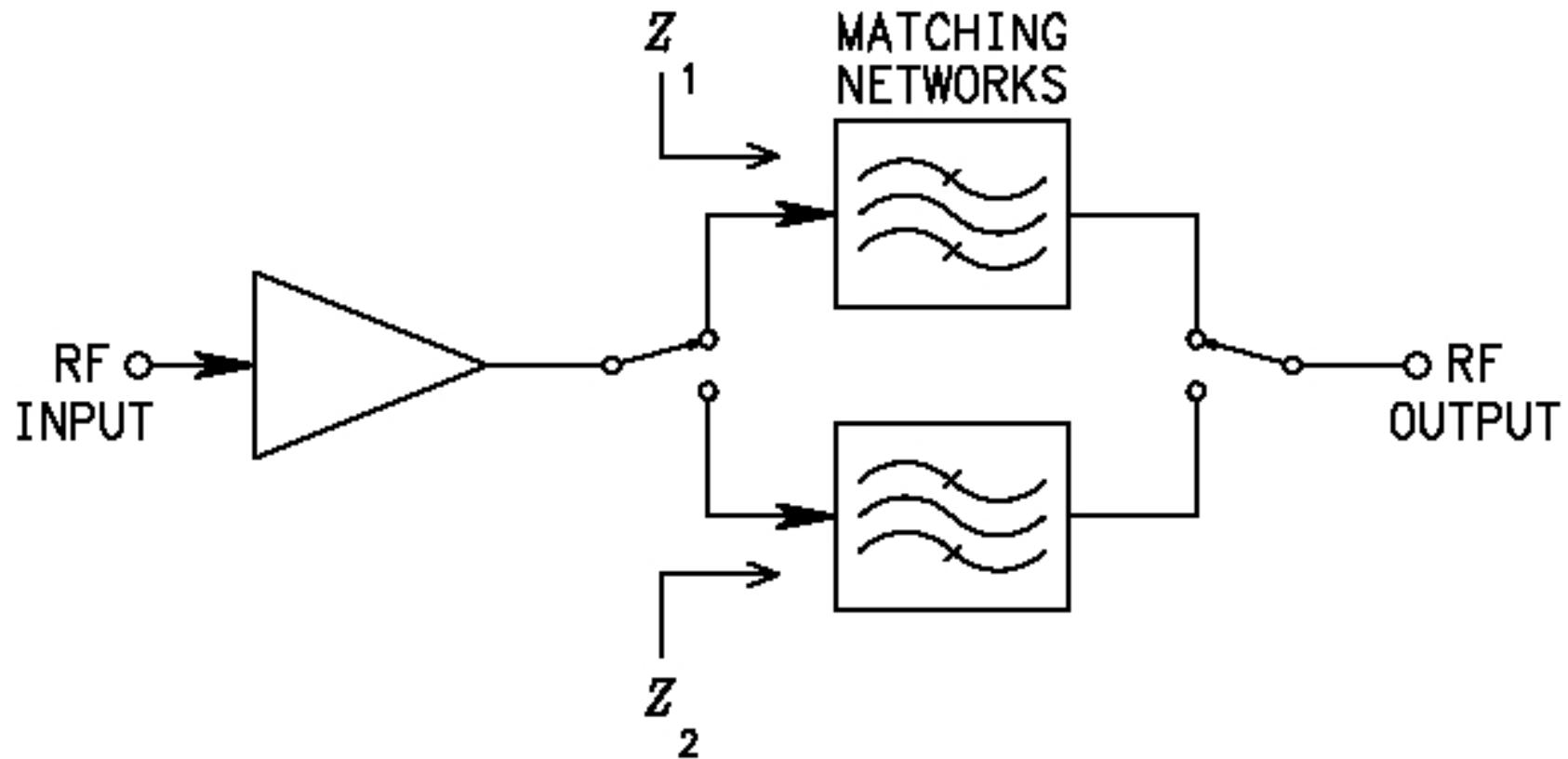

- High impedance → low power
- Low impedance → high power
- Matched both cases

MULTIPLE SWITCHED PAs

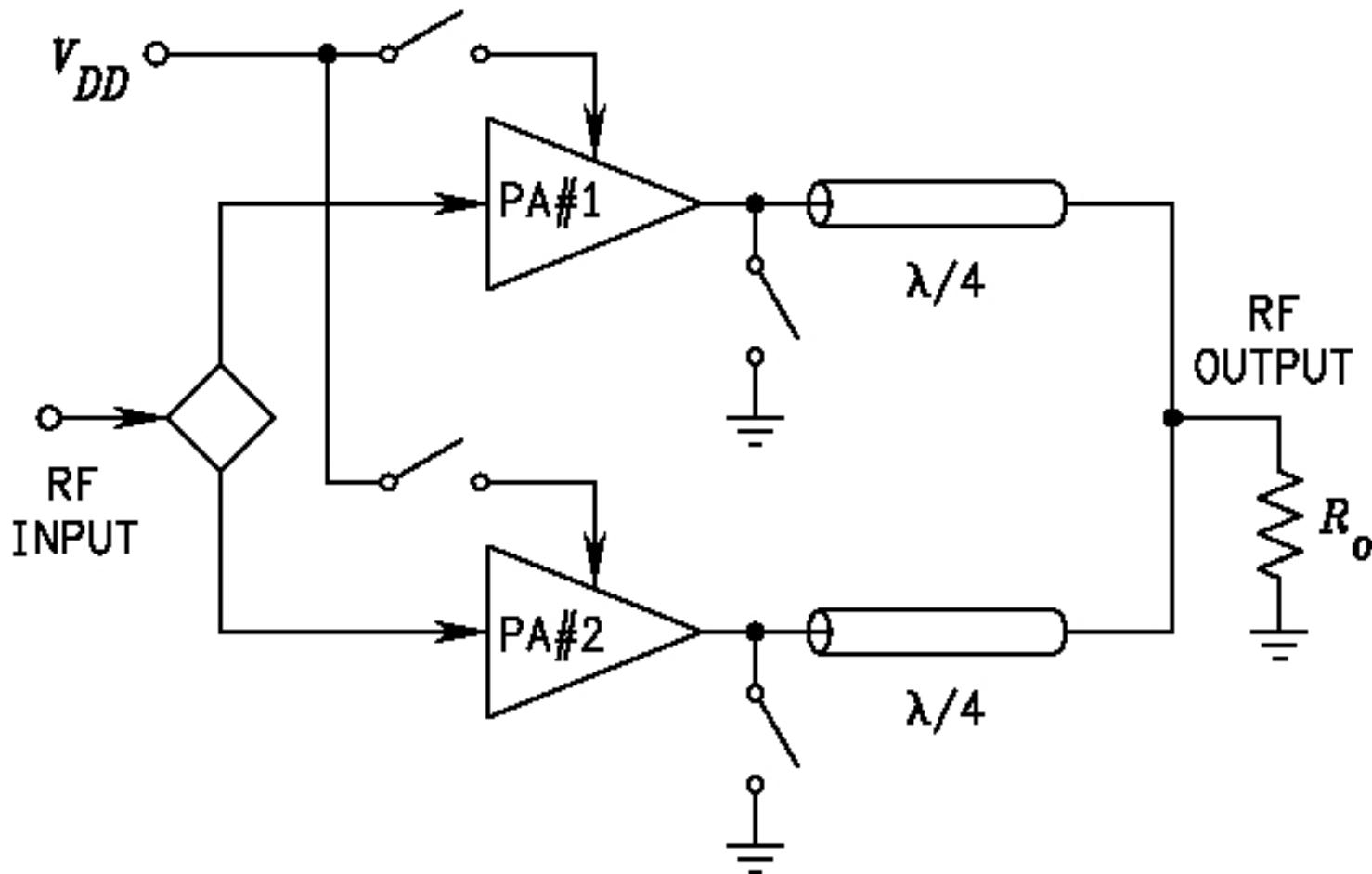

- Number of PAs active $\sim P_{o\text{PEP}}$
- Short PA output → Decouple from output

CONCLUSIONS

Variety of techniques available.

Significant improvements in average efficiency.

Each has advantages and disadvantages.

Combinations possible.

Interesting research to be done.

What is old is sometimes new again.